


## **CS221: Digital Design**

Waleed A. Yousef, Ph.D.,

Human Computer Interaction Lab.,  
Computer Science Department,  
Faculty of Computers and Information,  
Helwan University,  
Egypt.

October 25, 2017

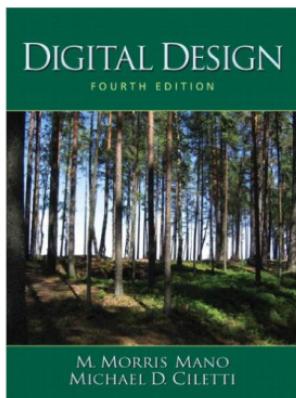**Lectures follow (and some figures are adapted from):**



Mano, M. M., Ciletti, M. D., 2007. Digital design, 4th Edition. Prentice-Hall, Upper Saddle River, NJ

**We will proceed as follows:**

- Fast introduction (few sections from Chapter 1).
- Detailed study of Chapters 2-7; very few sections will be skipped. At the end of each chapter Verilog code for some circuits will be explained.
- If time permits, Chapter 8 will be covered in full or in parts

# Course Objectives

This course combines three approaches to teach students Digital Design, which is the fundamental prerequisite to understand computer design and architecture:

1. Theoretical aspects of the subject will be covered in lectures, along with exercises in sections. Students, by the end of the course, should be able to design, analyze, and implement combinational and synchronous digital circuits.
2. A second objective is to teach students the digital design using a Hardware Descriptive Language (HDL). Students by the end of the semester will be able to analyze logic circuits with Verilog (one of the available HDLs).
3. A third objective is to develop the practical sense of the students through lab. experiments. Students will be able to implement logic circuits using breadboards and ICs.

# Contents

## Contents

		iii
<b>1</b>	<b>Introduction to Digital Systems</b>	<b>1</b>
1.9	From Binary Logic (Mathematics) to Logic Gates (Circuits) . . . . .	2
<b>2</b>	<b>Boolean Algebra and Logic Gates</b>	<b>9</b>
2.3	Axiomatic Definition of Boolean Algebra . . . . .	10
2.4	Basic Theorems and Properties of Boolean Algebra . . . . .	13
2.4.1	Operator Precedence . . . . .	15
2.5	Boolean Functions and Gate Implementation . . . . .	16
2.6	Canonical and Standard Forms . . . . .	20
2.6.1	Minterms and Maxterms . . . . .	20
2.6.2	Standard Forms . . . . .	24
2.7	Other Logic Operations . . . . .	26
2.8	Other Digital Logic Gates . . . . .	29
2.8.1	Extention to Multiple Inputs . . . . .	31
2.9	Integrated Circuits (ICs) . . . . .	34
2.9.1	Levels of Integration . . . . .	35
<b>3</b>	<b>Gate-Level Minimization</b>	<b>36</b>
3.1	Introduction . . . . .	37
3.2	The Map Method . . . . .	37
3.2.1	Two-Variable Map . . . . .	38

3.2.2	Three-Variable Map . . . . .	39
3.3	Four-Variable Map . . . . .	45
3.4	Five-Variable Map . . . . .	48
3.5	Product-of-Sums Simplifications . . . . .	50
3.6	Don't-Care Conditions . . . . .	52
3.6.1	More Examples on K-Map Simplifications . . . . .	53
3.7	Two-Level Implementation in NAND and NOR . . . . .	54
3.7.1	NOR Implementation . . . . .	56
3.9	Exclusive-OR (XOR) Function: revisit . . . . .	57
3.9.1	Parity Generation and Checking . . . . .	60
3.10	Hardware Descriptive Language (HDL) . . . . .	61
<b>4</b>	<b>Combinational Logic</b> . . . . .	<b>66</b>
4.1	Introduction: types of logic circuits . . . . .	67
4.2	Combinational Circuits . . . . .	68
4.3	Analysis Procedure . . . . .	69
4.4	Design Procedure . . . . .	70
4.4.1	Code Conversion Example . . . . .	70
4.5	Binary Adder-Subtractor . . . . .	72
4.5.1	Half Adder . . . . .	72
4.5.2	Full Adder . . . . .	73
4.5.3	Implementing FA using ONLY HA => modular design => very interesting . . . . .	74
4.5.4	Binary Adder: => more modular design => wonderful! . . . . .	75
4.5.5	Carry Propagation: complexity-speed trade off! . . . . .	76
4.5.6	Binary Subtractor . . . . .	78
4.5.7	Binary Adder-Subtractor . . . . .	79
4.6	Decimal Adder . . . . .	80
4.7	Binary Multiplier . . . . .	84
4.7.1	2-bit x 2-bit Multiplier . . . . .	84
4.7.2	3-bit x 4-bit Multiplier: How many bits? . . . . .	85
4.8	4-bit x 4-bit Magnitude Comparator . . . . .	86
4.9	$n \times 2^n$ Decoder: $D_i = m_i$ . . . . .	89
4.10	$2^n$ to $n$ Encoders . . . . .	92
4.10.1	Priority Encoder: $4 \times 2$ . . . . .	93
4.11	Multiplexers: $2^n \times 1$ . . . . .	94
4.11.1	Two-to-one-line Mux . . . . .	94
4.11.2	Four-to-one-line Mux . . . . .	95
4.11.3	Quadrable two-to-one-line Mux (block-reuse design) . . . . .	96
4.11.4	Boolean Function Implementation . . . . .	97
4.12	Demultiplexers (DEMUX) . . . . .	99
4.13	HDL Models of Combinational Circuits . . . . .	100

<b>5</b>	<b>Synchronous Sequential Logic</b>	<b>101</b>
5.1	Introduction . . . . .	102
5.2	Sequential Circuits . . . . .	103
5.3	Storage Elements: Latches (for asynchronous circuits) . . . . .	104
5.3.1	SR Latch . . . . .	104
5.3.2	D Latch (Transparent Latch) . . . . .	105
5.4	Storage Elements: Flip Flops (for synchronous circuits) . . . . .	106
5.4.1	Edge-Triggered D Flip-Flop . . . . .	107
5.4.2	Other Flip-Flops: JK and T Flip-Flops . . . . .	108
5.4.3	Direct Inputs (asynchronous reset) . . . . .	110
5.5	Analysis of Clocked Sequential Circuits (Synchronous Circuits) . . . . .	111
5.5.1	Mealy and Moore Models of FSM . . . . .	116
5.6	HDL Models of Sequential Circuits . . . . .	117
5.7	State Reduction and Assignments (needed for design) . . . . .	118
5.8	FSM: a generic preview . . . . .	120
5.8.1	Rigorous Mathematical Definition (Rosen, 2007, Ch. 12) . . . . .	120
5.8.2	FSM and Languages: . . . . .	121
5.9	Design Procedure . . . . .	122
<b>6</b>	<b>Registers and Counters</b>	<b>128</b>
6.1	Registers ( $n$ -bits, with parallel load) . . . . .	129
6.2	Synchronous Counters . . . . .	130
6.2.1	Binary Counters . . . . .	130
6.2.2	Up-Down Binary Counter . . . . .	131
6.2.3	BCD Counter . . . . .	132
6.2.4	Binary Counter with Parallel Load . . . . .	133
6.3	Shift Registers . . . . .	135
6.3.1	Serial Transfer (compare to parallel registers 6.1) . . . . .	136
6.3.2	Serial Addition . . . . .	137
6.3.3	Universal Shift Register . . . . .	139
6.4	Ripple Counters . . . . .	140
6.4.1	Binary Ripple Counters (all counts exist) recall synchronous 6.2.1	140
6.4.2	BCD Ripple Counters . . . . .	142
6.5	Other Counters . . . . .	143
6.5.1	Ring Counters . . . . .	143
6.5.2	Johnson Counter . . . . .	144
6.6	HDL for Registers and Counters . . . . .	145
<b>7</b>	<b>Memory and Programmable Logic</b>	<b>146</b>
7.1	Introduction . . . . .	147
7.2	Random-Access Memory (RAM): block-design . . . . .	148

7.3	Memory Decoding . . . . .	149
7.3.1	Internal Construction of 1-bit RAM . . . . .	149
7.3.2	Coincident Decoding . . . . .	151
7.3.3	Address Multiplexing . . . . .	152
7.4	Error Detection and Correction . . . . .	153
7.5	Read-Only Memory (ROM): non-volatile . . . . .	154
7.6	Programmable Array Logic (PAL) . . . . .	157
7.7	Programmable Logic Array (PLA) . . . . .	157
7.8	Sequential Programmable Devices: (more advanced topics) . . . . .	158
<b>8</b>	<b>Design at the Register Transfer Level: (a gate to "Computer Organization")</b>	
8.1	Introduction . . . . .	160
8.2	Register Transfer Language (RTL) . . . . .	161
8.3	Register Transfer Language (RTL) in HDL . . . . .	162
8.4	Algorithmic State Machines (ASMs) . . . . .	163
8.5	Design Example . . . . .	164
<b>A</b>	<b>Numbering System and Binary Numbers</b>	<b>A-1</b>
<b>B</b>	<b>Boolean Algebra</b>	<b>B-2</b>
<b>C</b>	<b>Digital Integrated Circuits (ICs)</b>	<b>C-3</b>

## Bibliography

## **Chapter 1**


# **Introduction to Digital Systems**

## 1.9 From Binary Logic (Mathematics) to Logic Gates (Circuits)


From what we have studied in Discrete Mathematics, we have the following basic three logic functions:

### *Truth Tables of Logical Operations*


		AND		OR		NOT	
$x$	$y$	$x \cdot y$		$x$	$y$	$x + y$	
0	0	0		0	0	0	
0	1	0		0	1	1	
1	0	0		1	0	1	
1	1	1		1	1	1	

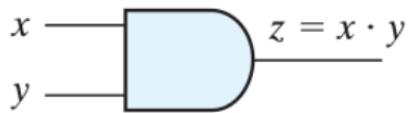

(a) Two-input AND gate

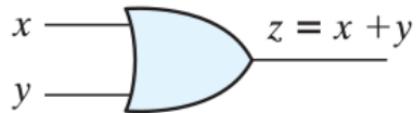


(b) Two-input OR gate

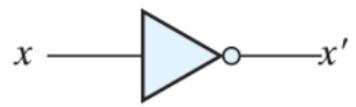


(c) NOT gate or inverter




 

(a) Three-input AND gate

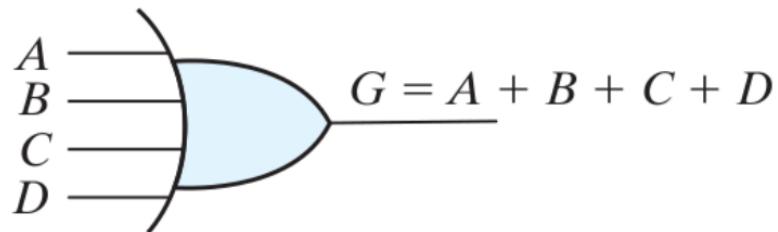


(b) Four-input OR gate

 

# Revisiting Course Objectives

## Theory (hands on paper)








 


## Simulation using Verilog

```
// Verilog model: Simple_Circuit
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;

    and   G1 (w1, A, B); // Optional gate instance
    not   G2 (E, C);
    or    G3 (D, w1, E);
endmodule
```

## Hardware Implementation

        

## **Chapter 2**

# **Boolean Algebra and Logic Gates**

## 2.3 Axiomatic Definition of Boolean Algebra

**Definition 1 :**

- Denote *True* and *False* by 1 and 0 that represent  $V_{cc}$  and 0 voltages.
- A **bit** (*binary digit*) is a symbol of these two values.
- A *Boolean Variable* is a variable that is either *True* or *False* (or simply 1 or 0); hence a bit.
- Given a set  $B = 0, 1$ , the three operators  
 $\cdot$ (AND),  $+$ (OR),  $'$ (NOT) are defined by:
- A *truth table* is the table that represents all the possible combinations of the input to a logical (Boolean) function.

$x$	$y$	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

$x$	$x'$
0	1
1	0

$x$	$y$	$x \cdot y$	$x$	$y$	$x + y$	$x$	$x'$
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1	1	0
1	1	1	1	1	1		

**Claim 2 (Boolean Postulates Come “Dual”)** :

1. *Closure: the structure is closed w.r.t.  $+$ ,  $\cdot$ .*

2. *Identity element:*

a)  $0 + x = x.$

b)  $1 \cdot x = x.$

3. *Commutative:*

a)  $x + y = y + x.$

b)  $x \cdot y = y \cdot x.$

4. *Distributive:*

a)  $x \cdot (y + z) = x \cdot y + x \cdot z.$

b)  $x + (y \cdot z) = (x + y)(x + z).$

5. *Complement:*

a)  $x + x' = 1.$

b)  $x \cdot x' = 0$

**Proof. :**

1. is clear from truth table above.
2. by simple truth table:
3. is from definition.
4. by constructing the truth table below:
5. from very simple truth table

$x$	$y$	$z$	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

## 2.4 Basic Theorems and Properties of Boolean Algebra

**Theorem 3 (dual postulates and theorems) :**

### *Postulates and Theorems of Boolean Algebra*

---

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

---

**Proof.** (algebraically and by truth table. Some algebraic proofs are tedious and truth table is sufficient):

**Theorem 1(a) algebraically :**

Statement	Justification
$x + x = (x + x) \cdot 1$	postulate 2(b)
$= (x + x)(x + x')$	5(a)
$= x + xx'$	4(b)
$= x + 0$	5(b)
$= x$	2(a)

**Theorem 1(a) by truth table :**

**Theorem 1(b) algebraically :**

Statement	Justification
$x \cdot x = xx + 0$	postulate 2(a)
$= xx + xx'$	5(b)
$= x(x + x')$	4(a)
$= x \cdot 1$	5(a)
$= x$	2(b)

**Theorem 1(b) by truth table :**

**Theorem 2(a-b)** : proof is very similar to above.

**Theorem 6(a)** : algebraically

$$\begin{aligned}
 x + xy &= x \cdot 1 + xy \\
 &= x \cdot (1 + y) \\
 &= x \cdot 1 \\
 &= x
 \end{aligned}$$

### Theorem 5(a) DeMorgan : truth table

x	y	$x + y$	$(x + y)'$	$x'$	$y'$	$x'y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

**Theorem 4 (Generalization)** . It can be easily shown that Theorems 4, 5 in the above table are generalize to more than 2 variables.

**Proof.** is straightforward by mathematical induction.

### Example 5

$$(A_1 + A_2 + \cdots + A_n)' = A'_1 A'_2 \cdots A'_n$$
$$(A_1 A_2 \cdots A_n)' = A'_1 + A'_2 + \cdots + A'_n.$$

### 2.4.1 Operator Precedence

(), NOT, AND, OR:

### Example 6

$$x + y \cdot (x + z)'$$

## 2.5 Boolean Functions and Gate Implementation

**Example 7** Evaluate and implement the functions:

$$F_1 = x + y'z$$



$$F_2 = x'y'z + x'yz + xy'$$

**Hint: be smart in filling the truth table:**

Truth Tables for  $F_1$  and  $F_2$

x	y	z	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0


**Hint: draw the circuits elegantly:**

  

 **Simplify the function to simplify the circuit; why?**

$$\begin{aligned}F_2 &= x'y'z + x'yz + xy' \\&= x'z(y' + y) + xy' \\&= x'z + xy',\end{aligned}$$

which has only 4 literals, where a literal is a single variable (complemented or un-complemented).



**Less gates (HW) means:**

- low cost.
- low power consumption.
- simpler implementation.

**Simplifying functions is by:**

- algebraic manipulation (this chapter)
- K-map (next chapter)
- computer programs for many-input functions

**Example 8** Simplify the following function to a minimum number of literals:

$$\begin{aligned}F_1 &= x(x' + xy) \\&= xx' + xxy \\&= 0 + xy = xy.\end{aligned}$$

$$\begin{aligned}F_2 &= xy + x'z + yz \\&= xy + x'z + xyz + x'y'z \\&= xy(1+z) + x'z(1+y) \\&= xy + x'z.\end{aligned}$$

$$\begin{aligned}F_3 &= (x(y'z' + yz))' \\&= x' + (y'z' + yz)' \\&= x' + (y+z)(y'+z') \\&= x' + yz' + y'z.\end{aligned}$$

**Hint: for simplicity apply DeMorgan by duality followed by inverting each literal:**

### **Example 9**

$$F_3 = x(y'z' + yz)$$

$$\text{dual of } F_3 = x + (y' + z')(y + z)$$

$$F'_3 = x' + (y + z)(y' + z').$$

## 2.6 Canonical and Standard Forms

### 2.6.1 Minterms and Maxterms

Minterms and Maxterms for Three Binary Variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	$m_0$	$x + y + z$	$M_0$
0	0	1	$x'y'z$	$m_1$	$x + y + z'$	$M_1$
0	1	0	$x'yz'$	$m_2$	$x + y' + z$	$M_2$
0	1	1	$x'yz$	$m_3$	$x + y' + z'$	$M_3$
1	0	0	$xy'z'$	$m_4$	$x' + y + z$	$M_4$
1	0	1	$xy'z$	$m_5$	$x' + y + z'$	$M_5$
1	1	0	$xyz'$	$m_6$	$x' + y' + z$	$M_6$
1	1	1	$xyz$	$m_7$	$x' + y' + z'$	$M_7$

- a minterm (or maxterm) equals one (or zero) only at one combination.
- the minterm (or maxterm) subscript is the order and value of this combination.
- order of variables is very important!
- $m_i = M'_i$ .
- E.g, what is the truth table of  $m_0$  and  $M_0$ ?
- Each function, then, can be expressed as either: **sum of minterms or product of maxterms!**

*Functions of Three Variables*

<b>x</b>	<b>y</b>	<b>z</b>	<b>Function <math>f_1</math></b>	<b>Function <math>f_2</math></b>
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**From Truth Table:**

**ORing (sum of) minterms**

$$\begin{aligned}
 f_1 &= \sum_{1 \text{ of } f_1} = \sum(1, 4, 7) = m_1 + m_4 + m_7 \\
 &= x'y'z + xy'z' + xyz, \\
 f'_1 &= \sum_{1 \text{ of } f'_1} = \sum_{0 \text{ of } f_1} = \sum(0, 2, 3, 5, 6) = m_0 + m_2 + m_3 + m_5 + m_6.
 \end{aligned}$$

**ANDing maxterms**

$$\begin{aligned}
 f_1 &= \prod_{0 \text{ of } f_1} = \prod(0, 2, 3, 5, 6) = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 \\
 &= (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z), \\
 f'_1 &= \prod_{0 \text{ of } f'_1} = \prod_{1 \text{ of } f_1} = \prod(1, 4, 7) = M_1 M_4 M_7.
 \end{aligned}$$

**Conclusion:** For any function  $f$  equals 1 on the set  $1$  and 0 on the set  $0$ :

$$\sum_{1 \text{ of } f} = \prod_{0 \text{ of } f} \Rightarrow f,$$
$$\sum_{0 \text{ of } f} = \prod_{1 \text{ of } f} \Rightarrow f'.$$

This is obtainable, as well, from DeMorgan:

$$\begin{aligned} f &= \sum_1 \\ &= (m_i + m_j + \dots) \\ f' &= (m_i + m_j + \dots)' \\ &= m'_i \cdot m'_j \dots \\ &= M_i \cdot M_j \dots \\ &= \prod_1 \end{aligned}$$

**Gate Implementation**

$$f_1 = \sum(1, 4, 7) = m_1 + m_4 + m_7 = x'y'z + xy'z' + xyz$$

**Converting algebraic expression to: sum of minterms or product of maxterms**

**Example 10 (two variables)**

$$\begin{aligned} A &= A(B' + B) = AB' + AB \\ &= m_2 + m_3. \end{aligned}$$

**Example 11**


$$\begin{aligned} A &= A(B'C' + B'C + BC' + BC) \\ &= AB'C' + AB'C + ABC' + ABC \\ &= m_4 + m_5 + m_6 + m_7. \end{aligned}$$

## 2.6.2 Standard Forms


- Sum of minterms and product of maxterms are almost not minimized (because each term contains by construction all variables).
- We should minimize and keep it as sum of products (SOP) or product of sums (POS), because it is only two-level implementation; e.g.,

$$F_1 = y' + xy + x'y'z'$$

$$F_2 = x(y' + z)(x' + y + z')$$

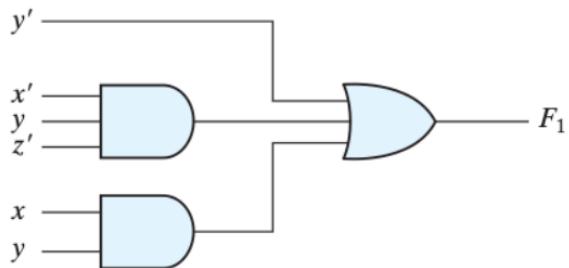

(a) Sum of Products

 


(b) Product of Sums

- Observe that, we do not consider inversion a level.
- This provides minimal signal delay and simpler implementation.
- So, implement any function as SOM (POM), then simplify to SOP (POS).


### Example 12 (2- vs. 3-level implementation)

$$F_3 = AB + C(D + E)$$

$$F_3 = AB + CD + CE.$$

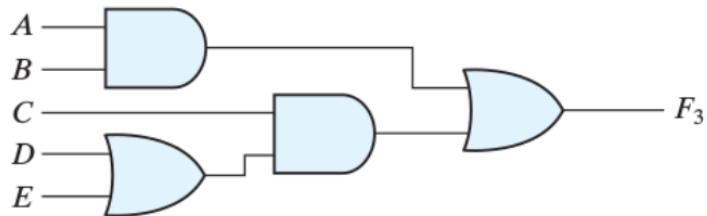

(a)  $AB + C(D + E)$

 

(b)  $AB + CD + CE$

## 2.7 Other Logic Operations

*Truth Tables for the 16 Functions of Two Binary Variables*

$x$	$y$	$F_0$	$F_1$	$F_2$	$F_3$	$F_4$	$F_5$	$F_6$	$F_7$	$F_8$	$F_9$	$F_{10}$	$F_{11}$	$F_{12}$	$F_{13}$	$F_{14}$	$F_{15}$
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1	

For  $n$  binary variables:

$$\begin{aligned}\text{number of functions} &= 2^{(\text{number of rows in truth table})} \\ &= 2^{2^n}.\end{aligned}$$

$$F_0 = 0,$$

$$F_1 = m_3 \quad = xy,$$

$$F_2 = m_2 \quad = xy',$$

$$F_3 = m_2 + m_3 \quad = xy' + xy \quad = x,$$

$$F_4 = m_1 \quad = x'y,$$

$$F_5 = m_1 + m_3 \quad = x'y + xy \quad = y,$$

$$F_6 = m_1 + m_2 \quad = x'y + xy' \quad = x \oplus y,$$

$$F_7 = M_0 \quad = x + y.$$

The other functions can be obtained, of course, by complementing the previous functions (Why?)

## Boolean Expressions for the 16 Functions of Two Variables

<b>Boolean Functions</b>	<b>Operator Symbol</b>	<b>Name</b>	<b>Comments</b>
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	$x$ and $y$
$F_2 = xy'$	$x/y$	Inhibition	$x$ , but not $y$
$F_3 = x$		Transfer	$x$
$F_4 = x'y$	$y/x$	Inhibition	$y$ , but not $x$
$F_5 = y$		Transfer	$y$
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	$x$ or $y$ , but not both
$F_7 = x + y$	$x + y$	OR	$x$ or $y$
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	$x$ equals $y$
$F_{10} = y'$	$y'$	Complement	Not $y$
$F_{11} = x + y'$	$x \subset y$	Implication	If $y$ , then $x$
$F_{12} = x'$	$x'$	Complement	Not $x$
$F_{13} = x' + y$	$x \supset y$	Implication	If $x$ , then $y$
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

**Special offer for Mathematics lovers:** from our study in Discrete Mathematics we have already learned that (Ch1. Rosen, 2007, P. 6):

Consider the sets  $\mathcal{X}, \mathcal{Y}$ , and any element  $e$ , and the indicators

$$x = I_{\mathcal{X}} = e \in \mathcal{X},$$

$$y = I_{\mathcal{Y}} = e \in \mathcal{Y},$$

then all the following are equivalent:

- $\mathcal{X} \subset \mathcal{Y}$  (**typo in book**),
- If  $x$  then  $y$ ,  $y$  if  $x$ ,  $y$  when  $x$ ,
- $x$  implies  $y$ ,  $y$  follows from  $x$ ,
- $x$  is sufficient for  $y$ ,  $y$  is necessary for  $x$ ,
- $F = M_2 = x' + y$ .

**HW:** what is the logic function  $F$  that represent the case that  $\mathcal{X} \cap \mathcal{Y} = \emptyset$  and  $\mathcal{X} \cup \mathcal{Y} \neq \Omega$ .

## 2.8 Other Digital Logic Gates

- From purely mathematical point of view: do we need more gates to implement other functions?

**Problem 13** (*Sec. 1.2 Rosen, 2007, Prob.: 43–45*): Show that NOT, OR, AND form a functionally complete collection of logical operators.

- **Motivation:** why, then, introducing new logic gates: NAND, NOR (next figure)? As we will see in Sec. 3.7:
  - NAND can represent the main three logic functions!
  - Similarly NOR (HW).
  - $\Sigma$  can be implemented **only** with NAND.
  - $\Pi$  can be implemented **only** with NOR.
  - Therefore, only NAND or NOR suffice.
  - Great to have uniform gate delay.
- We already know AND, OR, NOT gates, with direct hardware implementation. NAND, NOR have their hardware implementation as well.

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table border="1"> <thead> <tr> <th>x</th><th>y</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table border="1"> <thead> <tr> <th>x</th><th>y</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table border="1"> <thead> <tr> <th>x</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table border="1"> <thead> <tr> <th>x</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table border="1"> <thead> <tr> <th>x</th><th>y</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table border="1"> <thead> <tr> <th>x</th><th>y</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table border="1"> <thead> <tr> <th>x</th><th>y</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table border="1"> <thead> <tr> <th>x</th><th>y</th><th>F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

## 2.8.1 Extension to Multiple Inputs

AND, OR are directly extensible to multiple input from their commutative and associative laws:

$$(x + y) + z = x + (y + z),$$

$$(xy)z = x(yz).$$


Therefore, we **DEFINE**:

$$x + y + z = (x + y) + z = x + (y + z),$$

$$xyz = (xy)z = x(yz).$$



(a) Three-input AND gate

 



(b) Four-input OR gate

**Unfortunately:**  $\downarrow$  (NOR),  $\uparrow$  (NAND) are not associative:

$$(x \downarrow y) \downarrow z = ((x + y)' + z)' = (x + y)z' = xz' + yz',$$

$$x \downarrow (y \downarrow z) = (x + (y + z)')' = x'(y + z) = x'y + x'z.$$

  **HW:** prove the same for NAND  $\uparrow$ .



Hence, we have to **DEFINE:**

$$x \downarrow y \downarrow z = (x + y + z)',$$


$$x \uparrow y \uparrow z = (xyz)'. \quad \text{(De Morgan's law)}$$



(a) 3-input NOR gate



(b) 3-input NAND gate

 

(c) Cascaded NAND gates

## XOR Function

- Prove (by truth table) that it is commutative and associative; i.e.,

$$x \oplus y = y \oplus x,$$
$$x \oplus (y \oplus z) = (x \oplus y) \oplus z.$$


- Hence, we **DEFINE**:

$$x \oplus y \oplus z = (x \oplus y) \oplus z = x \oplus (y \oplus z)$$


- From its truth table, all the following are correct

- $x \oplus y = 1$  when only  $x$  or only  $y$  is 1.
- $x \oplus y = 1$  when  $x$  and  $y$  are different.
- $x \oplus y = 1$  when  $x$  and  $y$  have odd # of 1s.

 - Get the truth table of  $x \oplus y \oplus z$  as:



(a) Using 2-input gates

 

(b) 3-input gate

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


(c) Truth table

**Therefore**, the third meaning is emphasized:



$x \oplus y \oplus z = 1$  when they have odd number of ones; (more coming on parity check)
 
## 2.9 Integrated Circuits (ICs)

- We design a digital circuit using theory, HDL, and HW implementation in lab. (breadboards, ...) using data-sheets on page ( 8)



  - After settling on particular design, this circuit can be fabricated on an IC using sophisticated engineering tools and industry
- 



## **2.9.1 Levels of Integration**

**Small-Scale Integration (SSI)** ~ 10 gates;

(Ch. 3)

**Medium-Scale Integration (MSI)** ~ 10 ~ 1000 gates;

(Ch. 4 and 6)

**Lare-Scale Integration (LSI)** ~ 10,000 gates;

(Ch. 7 and Computer Organization course.)

**Very-Larage-Scale Integration** ~ 100,000 gates;

(complex processors,...)

## **Chapter 3**

# **Gate-Level Minimization**

### 3.1 Introduction



Let's remember why minimization (page 17).

### 3.2 The Map Method

- K-map (named after Karnaugh) is a visual method, utilizing **visual power**.
- Difficult for more than 5 variables.
- Produces always SOP or POS expressions.

### 3.2.1 Two-Variable Map

0	0
0	1
1	0
1	1

  

Simplify the following functions both algebraically and with K-Map and observe the visual power:

$$F_1 = m_1 + m_2 + m_3$$

$$= x'y + xy' + xy$$



$$= xy + x'y + xy' + xy = y + x.$$

$$F_2 = m_3$$

$$= xy.$$

$$F_3 = m_0 + m_3$$


$$= x'y' + xy.$$

  

- Only one-bit (variable) change for any two adjacent squares!

### 3.2.2 Three-Variable Map

0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

 


- Only one-bit (variable) change for any two adjacent squares! Therefore, e.g.,

$$F = m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$$


- Make sure of number of **variables** (e.g.,  $m_2 + m_3$  for 2 or 3 variables) and their **order**

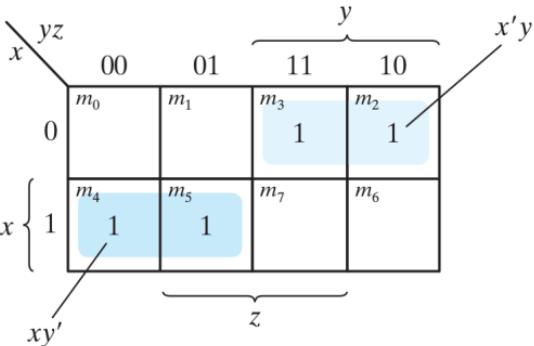**Example 14** : Simplify the function  $F(x, y, z) = \sum(2, 3, 4, 5)$ .



$$F = x'y + xy' = x \oplus y.$$

 **Example 15** Simplify  $F(x, y, z) = \sum(3, 4, 6, 7)$ . (**Hint:** look at the most isolated 1s first.)




$$\text{Note: } xy'z' + xyz' = xz'$$

$$F = xz' + yz.$$

**Example 16** : Consider the function  $F(x, y, z) = \sum(0, 2, 4, 5, 6)$ .

 1. Simplify  $F$ . (**Hint:** a group should have  $(2^m)$  ones and its resulting SOP has  $(n - m)$  literals.
2. Implement the function using AND, OR, NOT.
3. Observe the number of AND and OR gates (ignore inverters for now).



$$\begin{aligned}
 m_0 + m_2 + m_4 + m_6 &= x'y'z' + x'yz' + xy'z' + xyz' \\
 &= (x'y' + x'y + xy' + xy)z' \\
 &= (x'(y' + y) + x(y' + y))z' = (x' + x)z' = z'.
 \end{aligned}$$

(z' with the 4 combinations of x, y)  
(z' · Σ all Minterms of x, y = z')


---


$$F = xy' + z'.$$

**Example 17** Consider the function  $F = A'C + A'B + AB'C + BC$ .

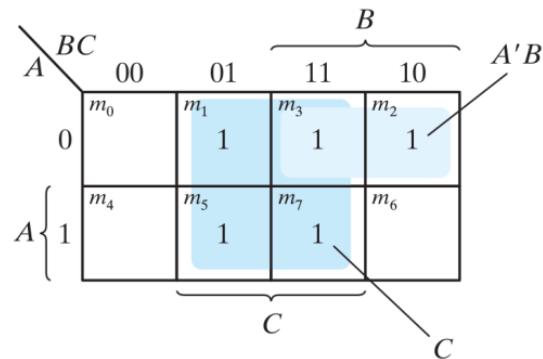1. Express the function as a sum of Minterms.
2. Find the minimal SOP expression.

**Hint:** each SOP term missing  $m$  literals will be expanded by  $2^m$  Minterms.



$$\begin{aligned}F(A, B, C) &= \sum(1, 2, 3, 5, 7) \\F &= C + A'B.\end{aligned}$$

## Golden Rules to Remember:

- Only one-bit (variable) change for any two adjacent squares!
- The boundaries are adjacent as well.
- A group of ones should be  $2^m$ , where  $m$  is the number of removed variables in this group (SOP), and the SOP will have  $n - m$  literals.
- Therefore, maximize the number of 1s in each group to minimize the number of literals in the SOP.
- Minimize the number of groups (the SOP terms).
- Therefore, start with the most isolated 1s.
- Make sure of number of **variables** and their **order**
- The number of literals in each group (SOP) is the number of inputs to its AND gate.
- The number of groups is the number of SOP terms is the number of AND gates is the number of inputs to the OR gate.
- All Minterms are covered.

### 3.3 Four-Variable Map


		yz		y		
		00	01	11		10
		$m_0$ $w'x'y'z'$	$m_1$ $w'x'y'z$	$m_3$ $w'x'yz$	$m_2$ $w'x'yz'$	
w	00	$m_4$ $w'xy'z'$	$m_5$ $w'xy'z$	$m_7$ $w'xyz$	$m_6$ $w'xyz'$	
	01	$m_{12}$ $wxy'z'$	$m_{13}$ $wxy'z$	$m_{15}$ $wxyz$	$m_{14}$ $wxyz'$	
	11	$m_8$ $wx'y'z'$	$m_9$ $wx'y'z$	$m_{11}$ $wx'yz$	$m_{10}$ $wx'yz'$	
	10					

w x  
y  
z

- Adjacency from top-bottom, right-left, and corners.
- Corners:**  $w$  and  $y$  took their 4 combinations at  $x = 0, z = 0: \Rightarrow$

$$\begin{aligned}
 m_0 + m_2 + m_8 + m_{10} &= w'x'y'z' + w'x'yz' + wx'y'z' + wx'yz' \\
 &= (w'y' + w'y + wy' + wy)x'z' \\
 &= x'z'.
 \end{aligned}$$

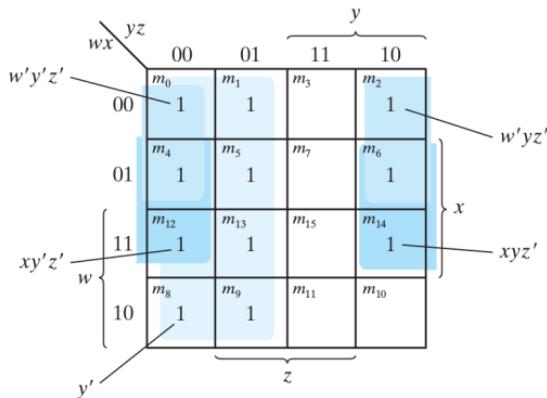**Example 18** Simplify the function  $F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$




Note:  $w'y'z' + w'yz' = w'z'$   
 $xy'z' + xyz' = xz'$

---


$$F = y' + w'z' + xz'.$$

 **Example 19** Simplify the function  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$ .





Note:  $A'B'C'D' + A'B'CD' = A'B'D'$   
 $AB'C'D' + AB'CD' = AB'D'$   
 $A'B'D' + AB'D' = B'D'$   
 $A'B'C' + AB'C' = B'C'$

---



$$F = B'D' + B'C' + A'CD'.$$

### 3.4 Five-Variable Map

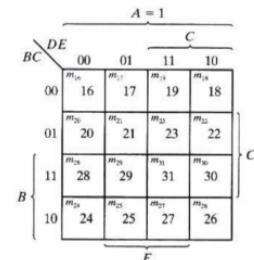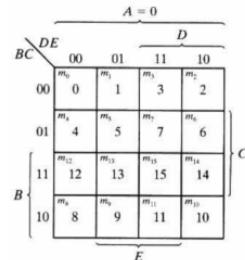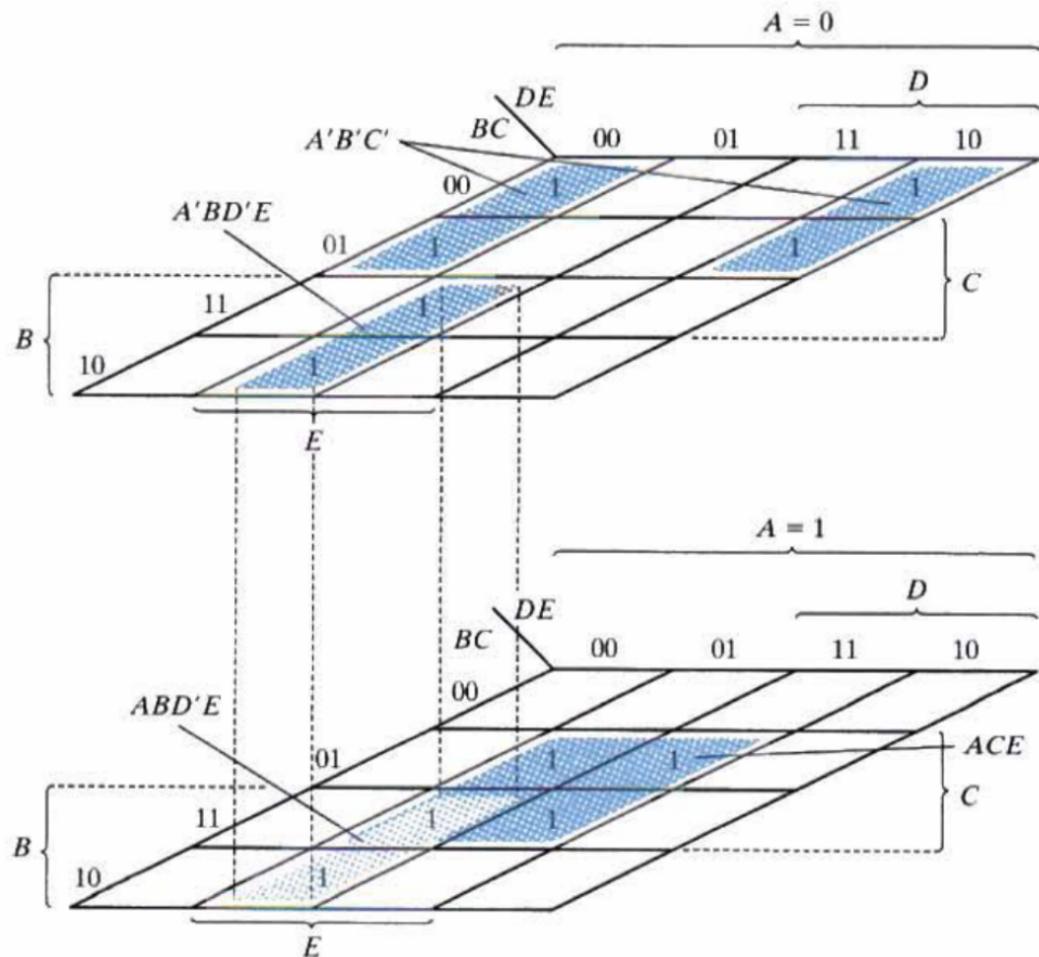

**Example 20** Simplify the function  $F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$ .


$$F = A'B'E' + BD'E + ACE.$$



### 3.5 Product-of-Sums Simplifications

 **Example 21** Simplify the function  $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$ . (**Hint:** Remember page (22)):

$$\sum_{1 \text{ of } f} = \prod_{0 \text{ of } f} \Rightarrow f, \quad \sum_{0 \text{ of } f} = \prod_{1 \text{ of } f} \Rightarrow f'.$$




Note:  $BC'D' + BCD' = BD'$

---



$$F = B'D' + B'C' + A'C'D = (A' + B')(C' + D')(B' + D).$$

## Two-Level Implementation

Remember: Section 2.6.2

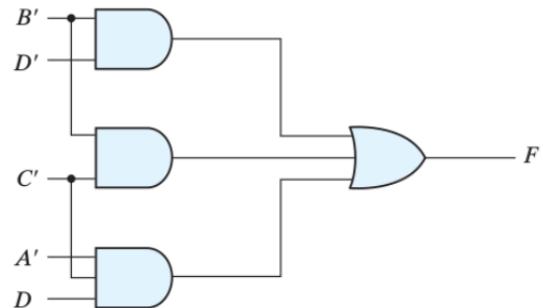 

$$(a) F = B'D' + B'C' + A'C'D$$




$$(b) F = (A' + B') (C' + D') (B' + D)$$

### 3.6 Don't-Care Conditions


- A combination of input that will not happen; so don't care about it. E.g., BCD.
- A combination of input at which we don't care about the output.

 **Example 22** Minimize  $F$  and find its expression in terms of Minterms:

$$F(w, x, y, z) = \sum(1, 3, 7, 11, 15); \quad d(w, x, y, z) = \sum(0, 2, 5).$$



(a)  $F = yz + w'x'$

 

(b)  $F = yz + w'z$

### 3.6.1 More Examples on K-Map Simplifications

1			1
1			1

1			
			1

1			1
x			1

1	1		
	1	1	1
		1	1

1	1	1	1
	1	1	1
		1	1
			1


1	1	1	1
	1	1	1
		1	1
x			1

1	1	1	1
1		1	1
1			1
1	1		1


### 3.7 Two-Level Implementation in NAND and NOR

- Recall that AND, OR, NOT are complete; they can implement any function.
- NAND, NOR can implement them as well.


**Example:**  $F = AB + CD$ .

 


(a)

 


(b)

 

(c)

 

(a) AND-invert



 


(b) Invert-OR

**Example 23** Minimize and implement, using only NAND gates the function.




**Hint:** remember to use a NAND for inverter to keep two-level implementations.

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$$

   

### 3.7.1 NOR Implementation

$$F = (A + B)(C + D)E$$

   

### 3.9 Exclusive-OR (XOR) Function: revisit


$$x \oplus y = xy' + x'y,$$

$$x \oplus 0 = x,$$


$$x \oplus 1 = x',$$

$$x \oplus x = 0,$$

$$x \oplus x' = 1.$$

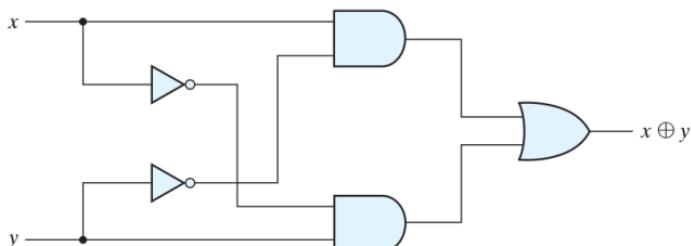

(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

$x$	$y$	$F$
0	0	0
0	1	1
1	0	1
1	1	0

## Three-Input XOR: (revise page 33)

		BC		B			
		00	01	11	10		
A		$m_0$	$m_1$	$m_3$	$m_2$		
0	0		1				
	1	$m_4$	$m_5$	$m_7$	$m_6$		


$C$

(a) Odd function  $F = A \oplus B \oplus C$


		BC		B			
		00	01	11	10		
A		$m_0$	$m_1$	$m_3$	$m_2$		
0	0		1				
	1	$m_4$	$m_5$	$m_7$	$m_6$		

$C$

 (b) Even function  $F = (A \oplus B \oplus C)'$



(a) 3-input odd function

 

(b) 3-input even function

- Of course, could be implemented with two-level ordinary implementation.

## Multi-Input XOR: (special offer for Mathematics lovers)

**Lemma 24** *The XOR function is an odd function for any arbitrary number of bits; i.e.,  $F = A_0 \oplus A_1 \dots A_n$  is 1 when  $(A_0 \dots A_n)$  have odd number of ones and 0 otherwise.*

**Proof.** We prove it by induction. For  $n = 1$ , it is true from the definition of XOR. Next, suppose the statement is true for some  $n$ . Then, for  $n + 1$ :


$$F_{n+1} = A_0 \oplus A_1 \dots A_{n+1}$$

$$F_{n+1} = F_n \oplus A_{n+1}.$$

$F_n$	$A_{n+1}$	$F_{n+1}$	$(A_0 \dots A_n)$	$(A_0 \dots A_{n+1})$
0	0	0	even	even
0	1	1	even	odd
1	0	1	odd	odd
1	1	0	odd	even

■
 
### Implementation of 4-input XOR using NANDs or only XORs




(a) Odd function  $F = A \oplus B \oplus C \oplus D$


### 3.9.1 Parity Generation and Checking

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
$x$	$y$	$z$	$p$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(a) 3-bit even parity generator

 

(b) 4-bit even parity checker



- With this implementation, checker works as generator if  $P = 0$ .
- HW:** How many 2-input XORs are needed to implement an even parity generator?

### **3.10 Hardware Descriptive Language (HDL)**

**The objective of the following few pages is to MOTIVATE you to self-start NOT to fully teach you**

- When circuits become complicated and hard to analyze either on paper or by HW implementation.
- The basic two languages supported by IEEE are VHDL and Verilog
- Verilog CD comes with the book, or you can download the SW and a free 6-months license from:  
<http://www.syncad.com/>

## A Basic Example

 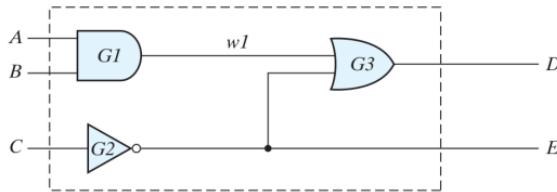

```
module Simple_Circuit (A, B, C, D, E);
    output      D, E;
    input       A, B, C;
    wire        wl;

    and         G1 (wl, A, B);
    not         G2 (E, C);
    or          G3 (D, wl, E);

endmodule
```

```
module Simple_Circuit_prop_delay (A, B, C, D, E);
    output      D, E;
    input       A, B, C;
    wire        wl;

    and         #(30) G1 (wl, A, B);
    not         #(10) G2 (E, C);
    or          #(20) G3 (D, wl, E);

endmodule
```

```
// Testbench for Simple_Circuit_prop_delay
'timescale 1 ns / 100 ps
module t_Simple_Circuit_prop_delay;
    wire D, E;
    reg A, B, C;

    Simple_Circuit_prop_delay M1 (A, B, C, D, E); // Instance name required

    initial
        begin
            A = 1'b0; B = 1'b0; C = 1'b0;
            #100 A = 1'b1; B = 1'b1; C = 1'b1;
            #100 $finish;
        end

    initial $monitor($time, "A = %b B= %b C = %b w1 = %b D = %b E = %b", A, B, C, D, M1.w1
                    , E);
endmodule
```

## Boolean Expressions

$$E = A + BC + B'D,$$
$$F = B'C + BC'D'.$$

```
// Verilog model: Circuit_Boolean_CA
module Circuit_Boolean_CA(E, F, A, B, C, D);
    output      E, F;
    input       A, B, C, D;
    assign E = A | (B & C) | (~B & D);
    assign F = (~B & C) | (B & ~C & ~D);
endmodule
```


## User-Defined Primitives

```
primitive UDP_02467 (D, A, B, C);  
    output D;  
    input A, B, C;  
// Truth table for D = f (A, B, C) = Sum (0, 2, 4, 6, 7);  
table
```

//	A	B	C	:	D // Column header
	0	0	0	:	1;
	0	0	1	:	0;
	0	1	0	:	1;
	0	1	1	:	0;
	1	0	0	:	1;
	1	0	1	:	0;
	1	1	0	:	1;
	1	1	1	:	1;

```
endtable  
endprimitive
```
 
```
// Verilog model: Circuit instantiation of Circuit_UDP_02467  
module Circuit_with_UDP_02467 (e, f, a, b, c, d);  
    output e, f;  
    input a, b, c, d;  
  
    UDP_02467 M0 (e, a, b, c);  
    and  
        (f, e, d); // instance name omitted  
endmodule
```




## **Chapter 4**

# **Combinational Logic**

## 4.1 Introduction: types of logic circuits

- **combinational:** output is function only of input (Ch. 4)
- **sequential:** output is function of input and previous output => MEMORY (Ch. 5–9)

## 4.2 Combinational Circuits

 

- Output is a function only of inputs.
- Therefore, outputs can be specified by only truth table or Boolean function.
- Of course,  $m \leq 2^{2^n}$ .
- In Ch. 4 we will employ the previous chapters to analyze, design, and simplify these circuits.
  - **Analysis:** given a circuit find the output as a function of input.
  - **Design:** given a certain functionality, design the circuit.

## 4.3 Analysis Procedure

- Make sure that the circuit has no feedback => combinational.
- Label outputs with meaningful names; then start propagating until you reach the output.

$$F_1 = T_3 + T_2$$

$$= F'_2 T_1 + ABC$$


$$= ABC +$$

$$(AB + AC + BC)'(A + B + C)$$

= :

$$= A'B'C + A'BC' + AB'C' + ABC$$

$$= \sum(1, 2, 4, 7).$$

 

A	B	C	$F_2$	$F'_2$	$T_1$	$T_2$	$T_3$	$F_1$
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

## 4.4 Design Procedure

1. Determine the number of inputs and outputs from the circuit functionality; then draw a block diagram without the internal details. This is exactly similar to function prototype in programming.
2. Derive a truth table.
3. Simplify the expression.
4. Implement the circuit.

### 4.4.1 Code Conversion Example



Design a circuit that converts from a BCD code to excess-3 code.

#### Motivation:


- Some circuits use excess-3 code and we need to feed this circuit with the right input.
- very easy to complement:  $9 - x$  is obtained by inverting the digits!

**Let's draft it on a clean page, then see the complete solution to save time.**


Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 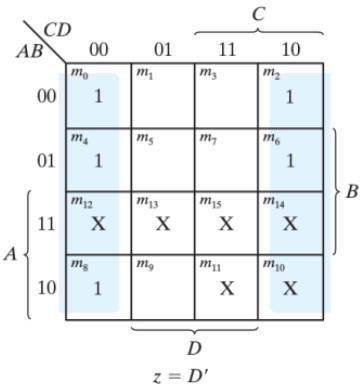

$$x = B'C + B'D + BC'D'$$

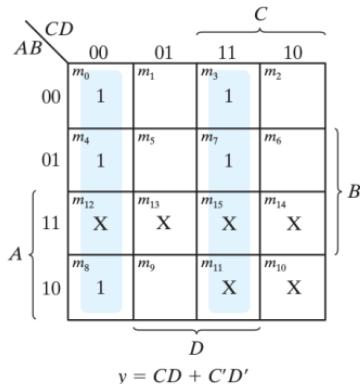

$$y = CD + C'D'$$

 


$$z = D'$$

## 4.5 Binary Adder-Subtractor


### 4.5.1 Half Adder

Half Adder

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

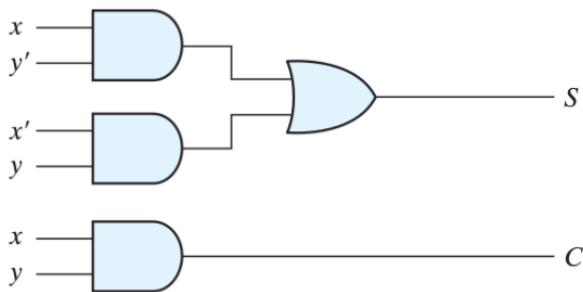

$$(a) S = xy' + x'y \\ C = xy$$

 


$$(b) S = x \oplus y \\ C = xy$$


## 4.5.2 Full Adder

### Full Adder



<b>x</b>	<b>y</b>	<b>z</b>	<b>C</b>	<b>S</b>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$(a) S = x'y'z + x'yz' + xy'z' + xyz$$

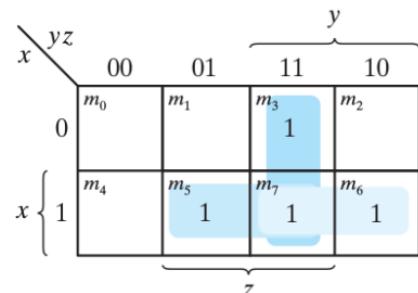

$$(b) C = xy + xz + yz$$

 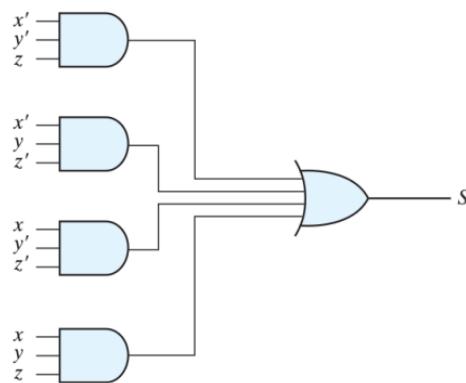

 
#### 4.5.3 Implementing FA using ONLY HA => modular design => very interesting



$$\begin{aligned} C_3 &= 0 \\ S &= S_2 = S_1 \oplus z \\ &= x \oplus y \oplus z \\ C &= S_3 = C_1 + C_2 \\ &= xy + S_1 z \\ &= xy + (x \oplus y)z \\ &= \vdots \\ &= \sum(3, 5, 6, 7) \end{aligned}$$

#### 4.5.4 Binary Adder: => more modular design => wonderful!


<b>Subscript <math>i</math>:</b>	<b>3</b>	<b>2</b>	<b>1</b>	<b>0</b>	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

 

**Hint:**

- without observing this modularity, it would be extremely difficult to design, e.g., 8-bit binary adder!
- carry subscript here is different from our previous example.
 
#### 4.5.5 Carry Propagation: complexity-speed trade off!



$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$


$$C_1 = G_0 + P_0 C_0$$




$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2$$
 
$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0.$$



  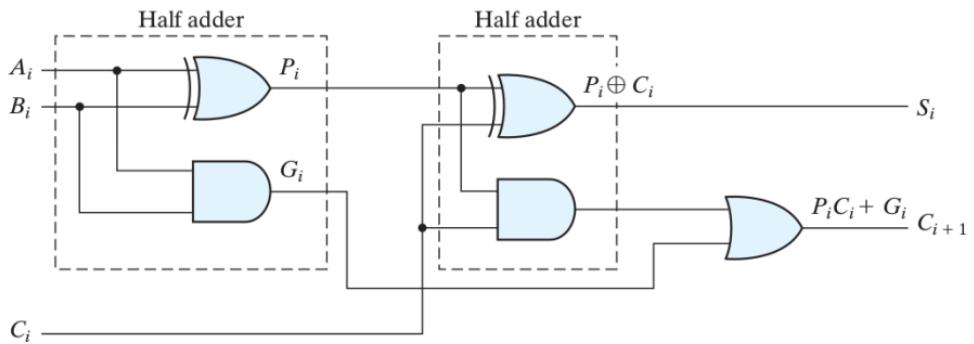

#### 4.5.6 Binary Subtractor

**Block Diagram level:**

From Appendix A (Binary Number System) we already know that for any  $n$ -bit numbers:

$$\begin{aligned}A - B &= A - B + 2^n - 2^n \\&= (A + (2^n - 1 - B) + 1) - 2^n \\&= (A + (\text{1's comp of } B) + 1) - 2^n \\&= (A + B' + 1) - 2^n.\end{aligned}$$

---

6	0110	0110	
2	0010	1101	
		1	
		10100	

---

**FAs level**

- For signed numbers, we use 2's Comp.
- Over-flow: when last two carries are different.

#### 4.5.7 Binary Adder-Subtractor

Back to truth table and K-Map:

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

x	y	f
0	0	0
0	1	1
1	0	A
1	1	B

0	1
A	B

0	1
A	x


0	0	1	1
x	A	x	x

M	Op	$x_i$	$y_i$	$C_0$
0	$A + B$	$A_i$	$B_i$	0
1	$A + B' + 1$	$A_i$	$B'_i$	1

$$x_i = A_i$$

$$y_i = M'B_i + MB'_i = M \oplus B_i$$

$$C_o = M.$$

 

## 4.6 Decimal Adder


**Design 1: very goofy**

5 functions, each:

$2^9 = 512$  rows!

cin	b3	b2	b1	b0	a3	a2	a1	a0	cout	s8	s4	s2	s1
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
				X									X


## Design 2: smarter but not yet

 

*Derivation of BCD Adder*

K	Binary Sum				BCD Sum					Decimal
	$Z_8$	$Z_4$	$Z_2$	$Z_1$	$C$	$S_8$	$S_4$	$S_2$	$S_1$	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

## Design 3: smartest!

 


Derivation of BCD Adder

K	Binary Sum				BCD Sum				Decimal	
	$Z_8$	$Z_4$	$Z_2$	$Z_1$	C	$S_8$	$S_4$	$S_2$	$S_1$	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


 
$$\begin{array}{r}
 C \quad a \ b \ c \ d \\
 \hline
 0 & 0 & 0 & 0 & 0 \\
 1 & 0 & 1 & 1 & 0
 \end{array}$$



## 4.7 Binary Multiplier


### 4.7.1 2-bit x 2-bit Multiplier



**Design 1:** truth table

**Design 2:** Let's think algorithmic
 
$$\begin{array}{r} & B_1 & B_0 \\ \begin{array}{r} A_1 \\ \hline A_0B_1 & A_0B_0 \end{array} & & \end{array}$$
$$\begin{array}{r} A_1B_1 & A_1B_0 \\ \hline C_3 & C_2 & C_1 & C_0 \end{array}$$



## 4.7.2 3-bit x 4-bit Multiplier: How many bits?


**Design 1: truth table (very goofy)**

**Design 2: smart**

	$B_3$	$B_2$	$B_1$	$B_0$		
	$A_2$	$A_1$	$A_0$			
0	0	0	$A_0B_3$	$A_0B_2$	$A_0B_1$	$A_0B_0$
0	0	$A_1B_3$	$A_1B_2$	$A_1B_1$	$A_1B_0$	0
0	$A_2B_3$	$A_2B_2$	$A_2B_1$	$A_2B_0$	0	0

---

$C_6$	$C_5$	$C_4$	$C_3$	$C_2$	$C_1$	$C_0$
-------	-------	-------	-------	-------	-------	-------

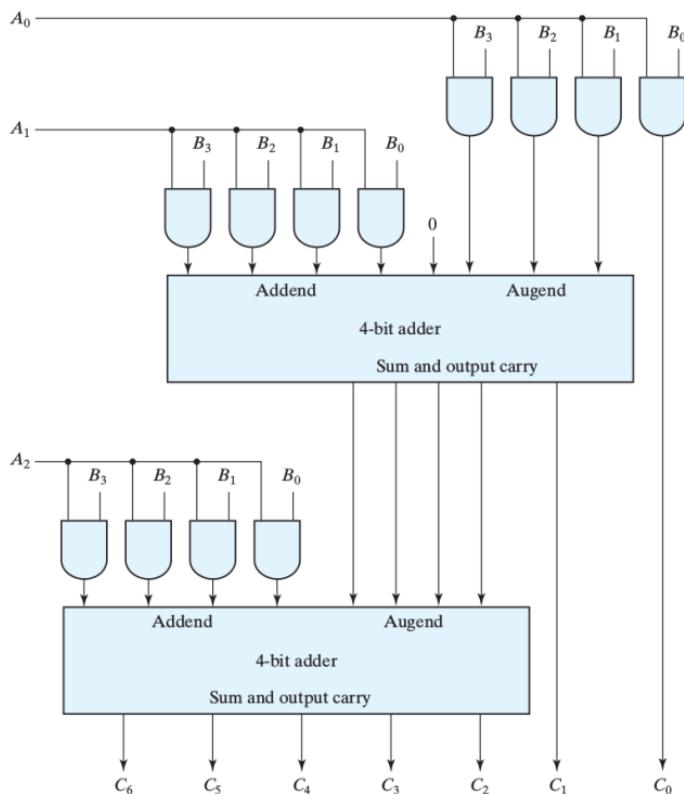

## 4.8 4-bit x 4-bit Magnitude Comparator

Design 1: truth table (very goofy).

Design 2: Let's go modular. design a 1-bit x 1-bit.

$A_0$	$B_0$	$L_0$	$S_0$	$E_0$
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

$$\begin{aligned}L_0 &= A_0 B'_0, \\S_0 &= A'_0 B_0, \\E_0 &= A'_0 B'_0 + A_0 B_0 \\&= (L_0 + S_0)'.\end{aligned}$$




For 4-bit comparator:

```
/* Algorithm for the logic: L = A > B
   A3 A2 A1 A0
   B3 B2 B1 B0
*/
L=(A3>B3) ||
(A3==B3)&&(A2>B2) ||
(A3==B3)&&(A2==B2)&&(A1>B1) ||
(A3==B3)&&(A2==B2)&&(A1==B1)&&(A0>B0)
```

$$L = L_3 + E_3 L_2 + E_3 E_2 L_1 + E_3 E_2 E_1 L_0$$

$$S = S_3 + E_3 S_2 + E_3 E_2 S_1 + E_3 E_2 E_1 S_0$$

$$E = E_3 E_2 E_1 E_0$$

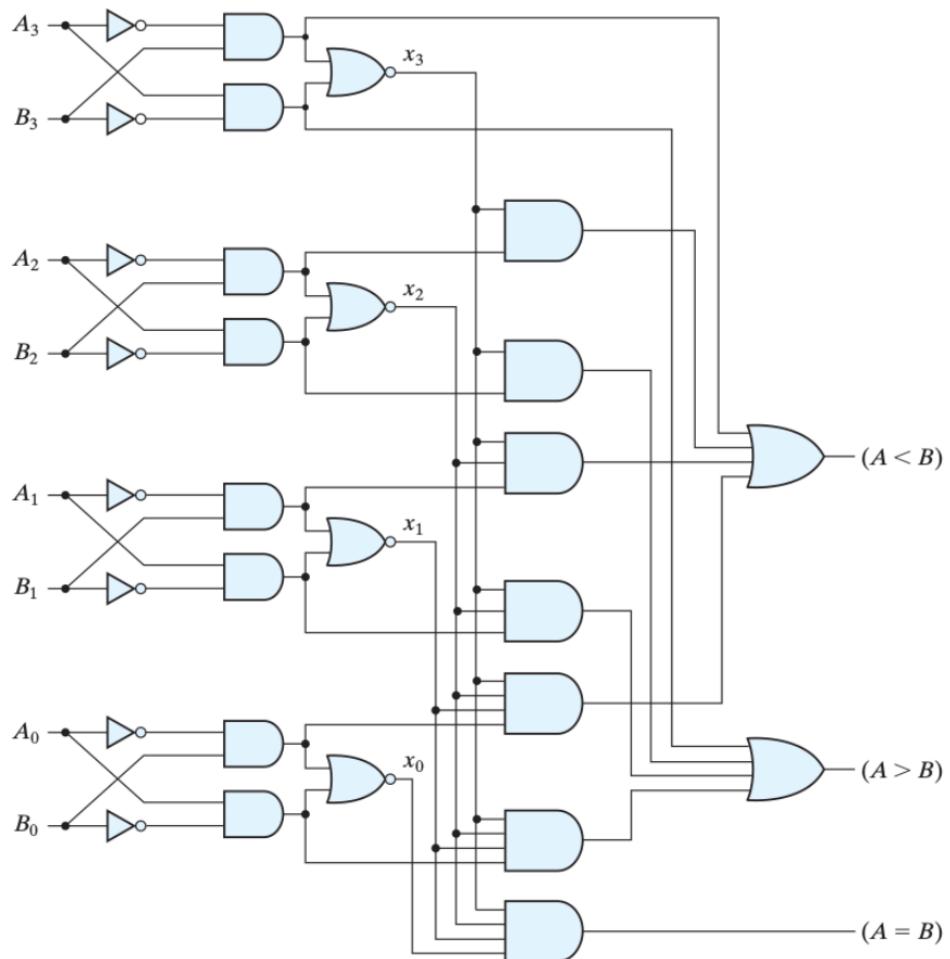

**Example 25** Design an 8-bit comparator.

**Design 1:** using the 1-bit comparator very similar to what we have done.


**Design 2:** using the 4-bit comparator.

$A_7$	$A_6$	$A_5$	$A_4$								
$B_7$	$B_6$	$B_5$	$B_4$	$A_3$	$A_2$	$A_1$	$A_0$	$B_3$	$B_2$	$B_1$	$B_0$

$$L = L_1 + E_1 L_0,$$


$$S = S_1 + E_1 S_0,$$

$$E = E_1 E_0.$$

 

**Is design 2 slower (propagation delay)? HW**
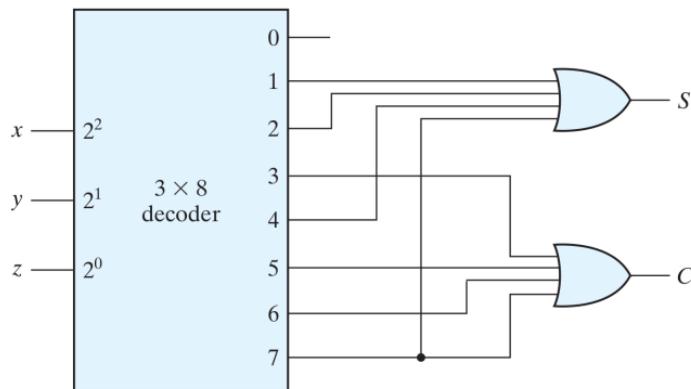
## 4.9 $n \times 2^n$ Decoder: $D_i = m_i$



$$S = \sum(1, 2, 4, 7)$$

$$C = \sum(3, 5, 6, 7)$$

$$K = \sum(0, 1, 2, 3, 4, 5)$$

$$K' = \sum(6, 7)$$

(# minterms  $> 2^n/2$ )


**inverted output and enabled decoders:**

E	$D_i$
0	0
1	$m_i$


$$D_i = Em_i$$

Truth Table of a Three-to-Eight-Line Decoder

Inputs			Outputs							
x	y	z	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

Therefore, we have:

 

E	Op.	$D_i$
0	Dsb	0
1	Enb	$m_i$


E	Op.	$D_i$
0	Enb	$m_i$
1	Dsb	0

E	Op.	$D_i$
0	Dsb	1
1	Enb	$M_i$

E	Op.	$D_i$
0	Enb	$M_i$
1	Dsb	1

**Example 26** Design a  $4 \times 16$  decoder using only  $3 \times 8$  decoders. **Hint:** take care of LSB and MSB.

w	x	y	z
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

 

we will see after studying multiplexer the connection to decoders!

## 4.10 $2^n$ to $n$ Encoders

*Truth Table of an Octal-to-Binary Encoder*

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- the opposite operation of decoders.

- we rely on no  $D_i = D_j = 1, i \neq j$ .

- no handling to  $D_i = 0 \forall i$

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7.$$

#### 4.10.1 Priority Encoder: 4 x 2

#	$D_3$	$D_2$	$D_1$	$D_0$	x	y	v
0	0	0	0	0	X	X	0
1	0	0	0	1	0	0	1
2-3	0	0	1	X	0	1	1
4-7	0	1	X	X	1	0	1
8-15	1	X	X	X	1	1	1

$$v = D_3 + D_2 + D_1 + D_0$$

X	0	0	0
1	1	1	1
1	1	1	1
1	1	1	1

$$x = D_3 + D_2$$


X	0	1	1
0	0	0	0
1	1	1	1
1	1	1	1

$$y = D_3 + D_1 D_2'$$

- $D_3$  is more prior than  $D_0$ .
- Xs in inputs are NOT don't care.
- V is 1 to indicate “Valid”.

**Example 27** Encode the comparator outputs L, S, E to X, Y such that:

cond.	X	Y
$A > B$	1	0
$A = B$	1	1
$A < B$	0	1

 

## 4.11 Multiplexers: $2^n \times 1$



How to use  $n$  selectors to select only one among  $2^n$  inputs?

### 4.11.1 Two-to-one-line Mux

**Motivation:** How to select between two variables (or more generally: two things)?

S	Y
0	$I_0$
1	$I_1$

$$Y = S'I_0 + SI_1$$

  



- Of course, we can make it Enable or Inv-Enable MUX; how?

#### 4.11.2 Four-to-one-line Mux

$S_1$	$S_0$	Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

$$\begin{aligned}
 Y &= I_0 S'_1 S'_0 + I_1 S'_1 S_0 + I_2 S_1 S'_0 + I_3 S_1 S_0 \\
 &= I_0 m_0 + I_1 m_1 + I_2 m_2 + I_3 m_3 \\
 &= \sum_{i=0}^{2^n-1} I_i m_i.
 \end{aligned}$$

  - $2^n \times 1$  MUX is an extension to  $n \times 2^n$  DEC (check Section 4.9)
- In Dec. :
  - All  $I_i$  where just the enable  $E$ .
  - No OR Gate.





### 4.11.3 Quadrable two-to-one-line Mux (block-reuse design)

**Design 1:**

$$Y_i = S' A_i + S B_i$$

S	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	$A_3$	$A_2$	$A_1$	$A_0$
1	$B_3$	$B_2$	$B_1$	$B_0$

  

#### 4.11.4 Boolean Function Implementation

- Given:  $F(x, y, z) = \sum(1, 2, 6, 7)$
- Implement it using  $4 \times 1$  MUX.

- Could we use  $2 \times 1$  MUX?

- For  $x = 0$


$$F = I_0 = y'z + yz'$$

- For  $x = 1$


$$F = I_1 = yz' + yz = y$$

$x$	$y$	$z$	$F$
0	0	0	0 $F = z$
0	0	1	1
0	1	0	1 $F = z'$
0	1	1	0
1	0	0	0 $F = 0$
1	0	1	0
1	1	0	1 $F = 1$
1	1	1	1

(a) Truth table

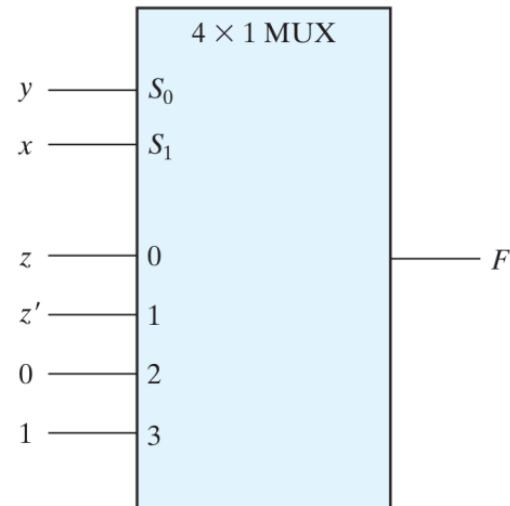


(b) Multiplexer implementation

 

**Example 28** : Implement the function  $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$  using  $8 \times 1$  MUX.


A	B	C	D	F
0	0	0	0	0 $F = D$
0	0	0	1	1
0	0	1	0	0 $F = D$
0	0	1	1	1
0	1	0	0	1 $F = D'$
0	1	0	1	0
0	1	1	0	0 $F = 0$
0	1	1	1	0
1	0	0	0	0 $F = 0$
1	0	0	1	0
1	0	1	0	0 $F = D$
1	0	1	1	1
1	1	0	0	1 $F = 1$
1	1	0	1	1
1	1	1	0	1 $F = 1$
1	1	1	1	1

 

## 4.12 Demultiplexers (DEMUX)

- Analogous to DEC-ENC could we have MUX-DEMUX?
- $2^n \times 1$  MUX  $\Rightarrow 1 \times 2^n$  DEMUX?
- Only the output  $F_i = I$  when selectors have a minterm value of  $i$

$$F_i = I m_i$$

 

- **HENCE:**  $1 \times 2^n$  DEMUX is nothing but Enabled  $n \times 2^n$  DEC, where the “Enable” is the input! (see Section 4.9)

## **4.13 HDL Models of Combinational Circuits**

# **Homework**

## **Chapter 5**

# **Synchronous Sequential Logic**

## 5.1 Introduction

- Remember the introduction of Section 4.1.
- In “Sequential” the new output is a function of its current value (“state”) and the input.



## 5.2 Sequential Circuits

**Asynchronous** : Ch. 9

- Element delay determines speed.
- Basic elements are “Latches”.
- Studied only if time permits.

**Synchronous** : Ch. (5–8)

  - Clock frequency (1GHz, 2GHz, etc.) determines speed.
- Basic elements are “Flip Flops” (but they are constructed from Latches)
- Clock design is an “Electronics” topic.
- Ch. 5–7 will be studied
- Ch. 8 is the introduction to “Computer Organization” course.



(a) Block diagram




(b) Timing diagram of clock pulses

## 5.3 Storage Elements: Latches (for asynchronous circuits)
 
### 5.3.1 SR Latch


- $Q(t+1) = f(Q(t), S, R)$
- We will prove  $Q$  and  $Q'$ .
- Value of  $Q \Rightarrow$  "state".
- $Q = 1 \Rightarrow$  "set".
- $Q = 0 \Rightarrow$  "reset".
- SR Latch with NAND implementation ( $S'R'$  Latch)
- SR Latch with Enable  $\Rightarrow$  "when"



S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(after  $S = 1, R = 0$ )  
(after  $S = 0, R = 1$ )  
(forbidden)


(b) Function table

 

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(after  $S = 1, R = 0$ )  
(after  $S = 0, R = 1$ )  
(forbidden)

(b) Function table

 


En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table
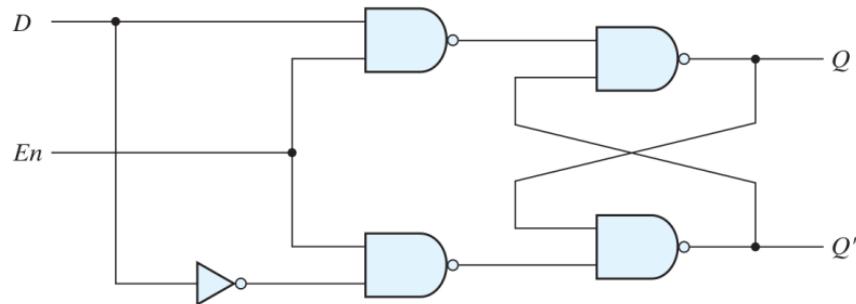
### 5.3.2 D Latch (Transparent Latch)

- A remedy to the forbidden condition => D Latch.
- D passes directly and stores into Q (transparent).
- What is the difference between D Latch and simply a wire!! => (memory)






(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table

### Graphic Symbols

   

## 5.4 Storage Elements: Flip Flops (for synchronous circuits)

- Problem with Enabled D Latch is output change during the whole positive Enable period!
- Response at ONLY edge Enabled is therefore required => CLOCK (positive or negative).



(a) Response to positive level



(b) Positive-edge response



(c) Negative-edge response

## 5.4.1 Edge-Triggered D Flip-Flop

**From Latches:**





- Master-Slave Flip-Flop
- This is negative-edge triggered.

**From Gates:**

**General Notes:**

- Either way, clock frequency (hence system speed) is confined to gate delay.
- $f = 1/T$
- The function table is the same as D-Latch with replacing En with Clk

Clk	D	Next State of Q
0/1	X	No change
↑	0	Q=0 reset
↑	1	Q=1 set

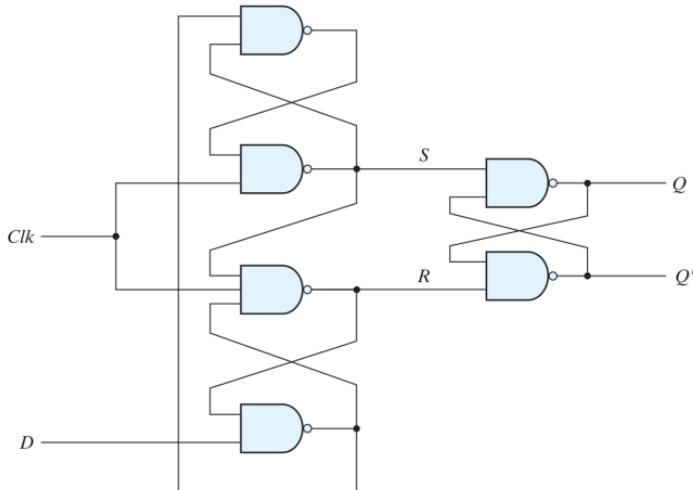   

## 5.4.2 Other Flip-Flops: JK and T Flip-Flops

- Let's understand them right now.
- How to reach the design of these and other Flip-Flops and convert from any Flip-Flop to others is detailed in Section 5.9

### JK Flip-Flop (from D Flip-Flop)

#### Input Equation


$$D = JQ' + K'Q$$

#### Characteristic Equation

$$\begin{aligned} Q(t+1) &= D \\ &= JQ'(t) + K'Q(t). \end{aligned}$$

#### Characteristic Table

J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset)
1	0	1 (set)
1	1	$Q'(t)$ (complement)

 

(a) Circuit diagram

(b) Graphic symbol


## T Flip-Flop (from D or JK Flip-Flops)

### Input Equation


$$D = T \oplus Q$$
 
### Characteristic Equation


$$\begin{aligned}Q(t+1) &= D \\&= T \oplus Q(t).\end{aligned}$$



(a) From JK flip-flop

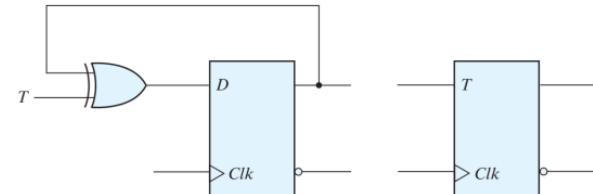

(b) From D flip-flop

 

(c) Graphic symbol

### Characteristic Table



T	$Q(t+1)$
0	$Q(t)$ (no change)
1	$Q'(t)$ (complement)

### 5.4.3 Direct Inputs (asynchronous reset)

- When power turns on, “state” is unknown.
- We need instant/direct/asynchronous reset.
- Here, active-low reset (similar to the Inv-En).

#### Function Table

R	Clk	D	Q	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

  


## 5.5 Analysis of Clocked Sequential Circuits (Synchronous Circuits)

We represent a sequential circuit (as well as combinational) by:

- circuit drawing.
- equation (“algebraic expression”, “state equation”, “transition equation”),
- table (“state table”, “transition table”) same as “truth table”, “characteristic table”, “functional table”


in addition:

 - state diagram (“Finite State Machine (FSM)”, “transition diagram”),
- timing diagram.




## 4,5- State Table and State Diagram (FSM)
 
### Example 29 (Analysis with D flip-flop)



Present State <b>A B</b>	Input <b>x</b>	Next State		Output <b>y</b>
		<b>A</b>	<b>B</b>	
0 0	0	0	0	0
0 0	1	0	1	0
0 1	0	0	0	1
0 1	1	1	1	0
1 0	0	0	0	1
1 0	1	1	0	0
1 1	0	0	0	1
1 1	1	1	0	0

 

Present State <b>A B</b>	Next State		Output	
	<b>x = 0</b>	<b>x = 1</b>	<b>x = 0</b>	<b>x = 1</b>
0 0	0 0	0 0	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

6- Timing Diagram:  $A(0) = 0$ ,  $B(0) = 0$ ,  $x = (1, 0, 1)$ .



**1- Input Equation (appropriate notation):**

$$D_A = Ax + Bx, \quad D_B = A'x.$$

**2- Flip-Flop Characteristic Equation:**

$$A(t+1) = D_A, \quad B(t+1) = D_B$$

**3- Output and State Equations:**

$$A(t+1) = Ax + Bx, \quad B(t+1) = A'x,$$

$$y = (A+B)x'.$$


A - - - - -

B - - - - -

x - - - - -

y - - - - -

### Example 30 (a simpler example) .

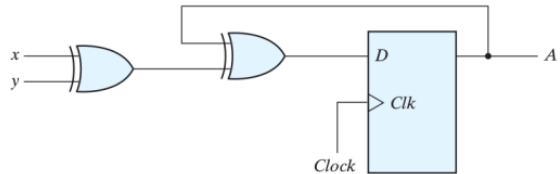

### 1- Input Equation (appropriate notation):

$$D_A = A \oplus x \oplus y$$

### 2- Flip-Flop Characteristic Equation:


$$A(t+1) = D_A$$

### 3- Output and State Equations:

$$A(t+1) = A \oplus x \oplus y$$

### 4,5- State Table and State Diagram (FSM)

Present state	Next state		
	$A$	$x$	$y$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

 

### 6- Timing Diagram: $A(0) = 0$ , $x = (1, 0, 1)$ , $y = (0, 1, 1)$ .




A - - - - -

x - - - - -


y - - - - -

## 4,5- State Table and State Diagram (FSM)
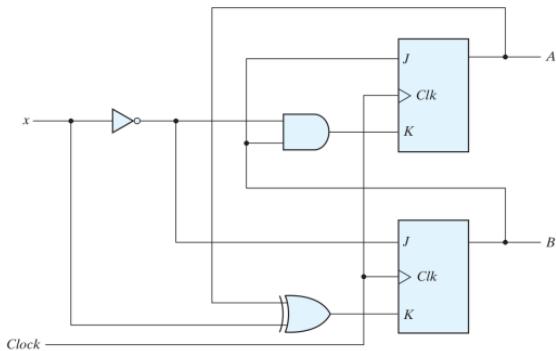
### Example 31 (Analysis with j-k flip-flop) .



Present State		Input <i>x</i>	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

 

### 1- Input Equation (appropriate notation):

$$J_A = B \quad K_A = Bx',$$

$$J_B = x' \quad K_B = A \oplus x.$$

### 2- Flip-Flop Characteristic Equation:

$$A(t+1) = J_A A' + K'_A A$$


$$B(t+1) = J_B B' + K'_B B$$

### 3- Output and State Equations:

$$A(t+1) = BA' + (Bx')'A = A'B + AB' + Ax$$


$$B(t+1) = x'B' + (A \oplus x)'B = B'x' + ABx + A'Bx'.$$
 
### 6- Timing Diagram: $A(0) = 0, B(0) = 0, x = (1, 0, 1).$




## 4,5- State Table and State Diagram (FSM)
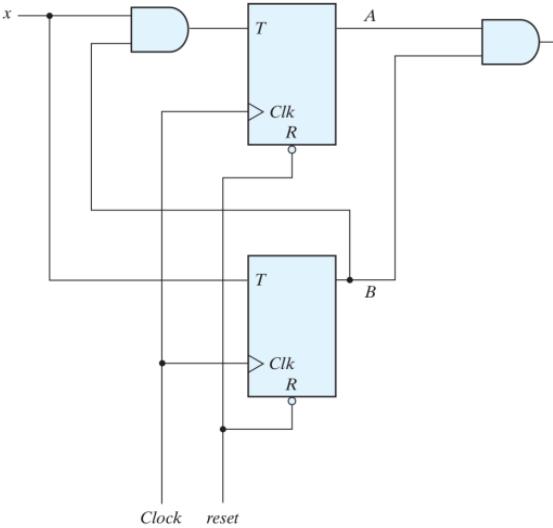
### Example 32 (Analysis with T flip-flop) .



Present State		Input $x$	Next State		Output $y$
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

6- Timing Diagram:  $A(0) = 0, B(0) = 0, x = (1, 0, 1).$



A - - - - -

x - - - - -

y - - - - -

1- Input Equation (appropriate notation): B

$$T_A = Bx, \quad T_B = x.$$

2- Flip-Flop Characteristic Equation:

$$A(t+1) = T_A \oplus A, \quad B(t+1) = T_B \oplus B$$

3- Output and State Equations:


$$A(t+1) = Bx \oplus A, \quad B(t+1) = x \oplus B,$$

$$y = AB.$$

## 5.5.1 Mealy and Moore Models of FSM
 
### Moore:




- Output is fully synchronized with flip-flops output and, of course, clock even if the input is not synced.


   
### Mealy:

- Output may change during the cycle if input changes!
- Input should be synchronized with clock (either with active or inactive edge)
- The moment right before the active edge is guaranteed to be correct.
- Very simple example:



$$D = x, \quad y = Ax, \quad A(0) = 0, \quad x = (1, 0).$$



## **5.6 HDL Models of Sequential Circuits**

# **Homework**
 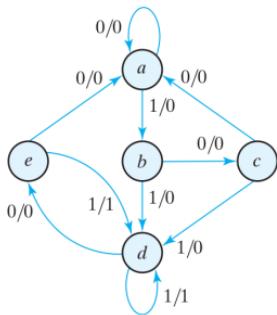
## 5.7 State Reduction and Assignments (needed for design)



State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
a	000	000	00001
b	001	001	00010
c	010	011	00100
d	011	010	01000
e	100	110	10000

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

# Flip-Flop Excitation Tables (inverse function)

## characteristic table & equation

T	$Q(t+1)$
0	$Q$ (no change)
1	$Q'$ (complement)

$$Q(t+1) = T \oplus Q$$

J	K	$Q(t+1)$
0	0	$Q$ (no change)
0	1	0 (reset)
1	0	1 (set)
1	1	$Q'$ (complement)

$$Q(t+1) = JQ' + K'Q.$$

D	$Q(t+1)$
0	0 (reset)
1	1 (set)

$$Q(t+1) = D$$

T	Q	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

J	K	Q	$Q(t+1)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Q	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Q	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

## 5.8 FSM: a generic preview

### 5.8.1 Rigorous Mathematical Definition (Rosen, 2007, Ch. 12)


**Definition 33 (Finite-State Machines with Outputs and Finite State Automata (without outputs)) :**

A Finite-State Machine (FSM)  $M = (S, I, O, f, g, s_0)$  consists of:

- $S$ , a finite set of states,
- $I$ , a finite input alphabet,
- $O$ , a finite output alphabet,
- $f : S \times I \rightarrow S$ , a transition function such that assigns to each state and input pair a new state,
- $g$ , an output function that assigns to each state and input pair and output, and
- $s_0$ , an initial state.

 **Example 34 (Vending Machine) :**

© The McGraw-Hill Companies, Inc. all rights reserved.



## 5.8.2 FSM and Languages:


- Language Recognition
- Compiler Design
- Natural Language Processing
- Formal Languages
- :

## Theory of Computation (Sipser, 2006)

1.3 REGULAR EXPRESSIONS 69
 
### EXAMPLE 1.58

In Figure 1.59, we convert the regular expression  $(a \cup b)^*aba$  to an NFA. A few of the minor steps are not shown.



### FIGURE 1.59

Building an NFA from the regular expression  $(a \cup b)^*aba$

Now let's turn to the other direction of the proof of Theorem 1.54.


### LEMMA 1.60

If a language is regular, then it is described by a regular expression.

**PROOF IDEA** We need to show that, if a language  $A$  is regular, a regular expression describes it. Because  $A$  is regular, it is accepted by a DFA. We describe a procedure for converting DFAs into equivalent regular expressions.

## 5.9 Design Procedure: (all is about FSM design; others are routine stuff)

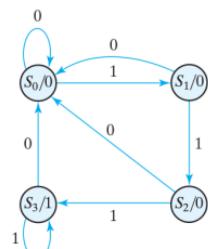Example 35 (Detect 3 ones in row (overlap)) .



State table, reduction, and assignment			
P.S.	N.S.	Y	
	$x = 0$	$x = 1$	
$S_0$	$S_0$	$S_1$	0
$S_1$	$S_0$	$S_2$	0
$S_2$	$S_0$	$S_3$	0
$S_3$	$S_0$	$S_3$	1

A	B	x	AB	y	D <sub>AD</sub>	J <sub>A</sub> K <sub>A</sub>	J <sub>B</sub> K <sub>B</sub>	excitation table
0	0	0	00	0		0X	0X	
0	0	1	01	0		0X	1X	
0	1	0	00	0		0X	X1	
0	1	1	10	0		1X	X1	
1	0	0	00	0		X1	0X	Q, Q(t+1)
1	0	1	11	0		X0	1X	JK
1	1	0	00	1		X1	X1	00
1	1	1	11	1		X0	X0	0X
								1X
								10
								X1
								X0

$$\begin{array}{c} Bx \\ \diagdown \quad \diagup \\ A \quad \begin{matrix} 00 & 01 & \overbrace{\quad \quad \quad}^B & 10 \\ m_0 & m_1 & & m_2 \\ \hline m_4 & m_5 & m_7 & m_6 \end{matrix} \\ \begin{matrix} 0 & \\ A \\ 1 \end{matrix} \end{array}$$



$D_A = Ax + Bx$

$$\begin{array}{c} Bx \\ \diagdown \quad \diagup \\ A \quad \begin{matrix} 00 & 01 & \overbrace{\quad \quad \quad}^B & 10 \\ m_0 & m_1 & m_3 & m_2 \\ \hline m_4 & m_5 & m_7 & m_6 \end{matrix} \\ \begin{matrix} 0 & \\ A \\ 1 \end{matrix} \end{array}$$

$D_B = Ax + B'x$


$$\begin{array}{c} Bx \\ \diagdown \quad \diagup \\ A \quad \begin{matrix} 00 & 01 & \overbrace{\quad \quad \quad}^B & 10 \\ m_0 & m_1 & m_3 & m_2 \\ \hline m_4 & m_5 & m_7 & m_6 \end{matrix} \\ \begin{matrix} 0 & \\ A \\ 1 \end{matrix} \end{array}$$

$y = AB$

  


### Example 36 (Detect 3 ones in row (with/without overlap) both (Moore and Mealy)) .

**overlap Moore**

 

**overlap Mealy**

 


compare to page 112



P.S.	N.S./Y
$x = 0$	$x = 1$
$S_0$	$S_0/0$
$S_1$	$S_0/0$
$S_2$	$S_0/0$
	$S_1/0$
	$S_2/0$
	$S_2/1$

**input sequence:** 011011110


**no overlap Moore**

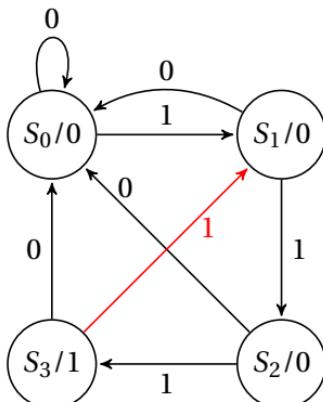

**no overlap Mealy**

  
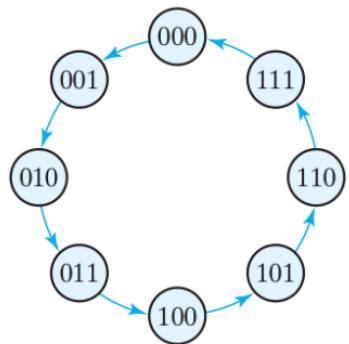
### Example 37 (Using a T FF, design a circuit that counts from 0 to 7. comp. to D and JK P. 109) .



Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

$Q$	$Q(t+1)$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

$A_2$	$A_1 A_0$		$A_1$	
	00	01	11	10
$A_2$	$m_0$	$m_1$	$m_3$	1
	$m_4$	$m_5$	$m_7$	1
$A_2$	$m_0$	$m_1$	$m_3$	$m_2$
	$m_4$	$m_5$	$m_7$	$m_6$

$A_0$

$T_{A2} = A_1 A_0$

$A_2$	$A_1 A_0$		$A_1$	
	00	01	11	10
$A_2$	$m_0$	1	$m_3$	1
	$m_4$	$m_5$	$m_7$	$m_6$
$A_2$	$m_0$	$m_1$	$m_3$	$m_2$
	1	1	1	1

$A_0$

$T_{A1} = A_0$


$A_2$	$A_1 A_0$		$A_1$	
	00	01	11	10
$A_2$	$m_0$	$m_1$	$m_3$	$m_2$
	1	1	1	1
$A_2$	$m_0$	$m_1$	$m_3$	$m_2$
	1	1	1	1

$x$


$T_{A0} = 1$

$$T_0 = 1$$
 
$$T_i = \prod_{j=0}^{J=i-1} A_j, \quad i > 0$$


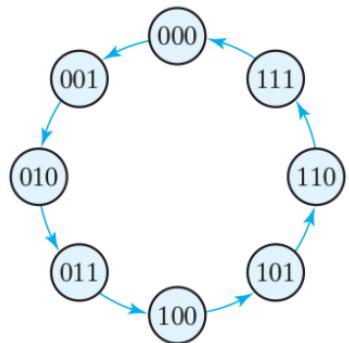
### Example 38 (Using a T FF, design a circuit that counts from 0 to 4 and check for unused states!) .



Present State			Next State			Flip-Flop Inputs			$Q$	$Q(t+1)$	$T$
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$			
0	0	0	0	0	1	0	0	1	0	0	0
0	0	1	0	1	0	0	1	1	0	1	1
0	1	0	0	1	1	0	0	1	1	0	1
0	1	1	1	0	0	1	1	1	1	1	1
1	0	0	1	0	1	0	0	1	0	1	1
1	0	1	1	1	0	0	1	1	0	1	1
1	1	0	1	1	1	0	1	1	1	0	1
1	1	1	0	0	0	1	1	1	1	1	0

0	0	1	0
1	X	X	X

$$T_{A_2} = A_2 + A_1 A_0$$

0	1	1	0
0	X	X	X

$$T_{A_1} = A_0$$



1	1	1	1
0	X	X	X

$$T_{A_0} = A'_2$$



**unused states analysis:**

PS.	$T$	N.S.
$A_2 A_1 A_0$	$T_{A_2} T_{A_1} T_{A_0}$	$A_2 A_1 A_0$
101	110	011
110	100	010
111	110	001

  **Example 39 (Detect 0101 with/without overlap) .**



  **Example 40 (Detect whether each 4 cycles contain 0101) .**



### **Example 41 (Convert from a JK flip-flop to T flip-flop) .**

*This is equivalent to: using JK flip-flop design a circuit whose state-table is the characteristic table of T flip-flop (both are essentially the same of course).*

**No need for transition diagram:**

T	Q	Q(t+1)	J	K	Q, Q(t+1)	JK
0	0	0	0	X	0 0	0 X
0	1	1	X	0	0 1	1 X
1	0	1	1	X	1 0	X 1
1	1	0	X	1	1 1	X 0

0	X
1	X

$$J = T$$

X	0
X	1

$$K = T$$



**Same as P. 109**

# **Chapter 6**

## **Registers and Counters**

**Same sections from book but in different order**
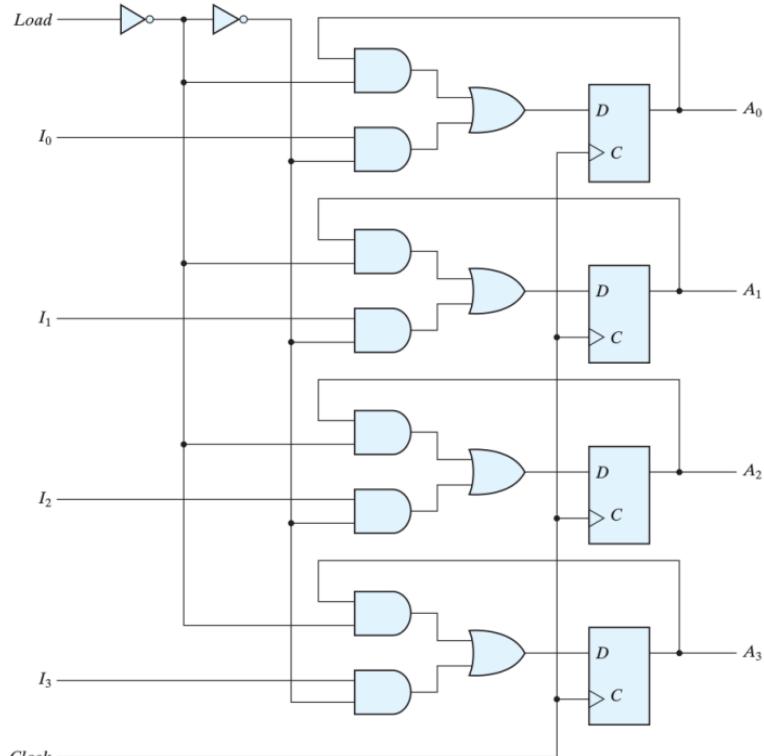 
## 6.1 Registers ( $n$ -bits, with parallel load)



**Info. transfer.**


**Load circuit: MUX.**

**Modular vs. discrete Logic**

L	function	$A_i(t+1)$	D	J	K	$D_i = L'A_i + LI_i$
0	no change	$A_i$	$A_i$	0	0	$J_i = LI_i,$
1	Load	$I_i$	$I_i$	$I_i$	$I'_i$	$K_i = LI'_i$

## 6.2 Synchronous Counters

### 6.2.1 Binary Counters

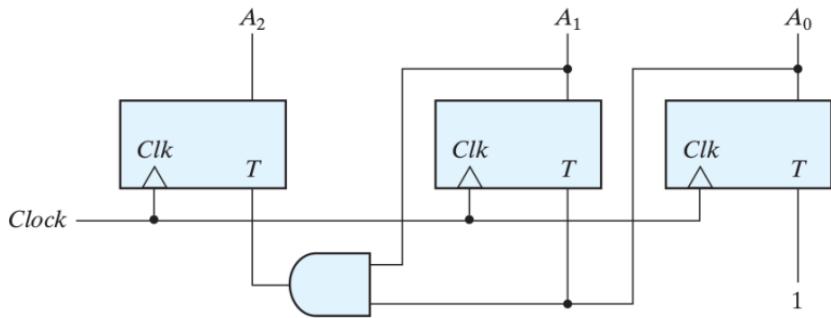

$$T_0 = 1$$

(Up/Down)


$$T_i = \prod_{j=0}^{J=i-1} A_j, \quad i > 0 \quad (\text{Up})$$

$$T_i = \prod_{j=0}^{J=i-1} A'_j, \quad i > 0 \quad (\text{Down})$$

- As in Example 37
- Clock could be +/-
- Other complementing FF (P. 109)
- Count-Down counter is immediate by:
- Count-enable (C)

C	Function	T
0	no change	0
1	count up	EQ

$T = C \cdot EQ$

 

## 6.2.2 Up-Down Binary Counter

U	D	Function	$T_i$
0	0	no change	0
0	1	down	$\prod_0^{i-1} A'_j, T_0 = 1$ (EqD)
1	x	up	$\prod_0^{i-1} A_j, T_0 = 1$ (EqU)



$$T_i = U'D \cdot EqD + U \cdot EqU,$$

$$T_1 = U'D + U = U + D$$

0	EqD
EqU	EqU

The controllers could be:

C	U	Function	$T_i$
0	x	no change	0
1	0	down	$\prod_0^{i-1} A'_j, T_0 = 1$ (EqD)
1	1	up	$\prod_0^{i-1} A_j, T_0 = 1$ (EqU)

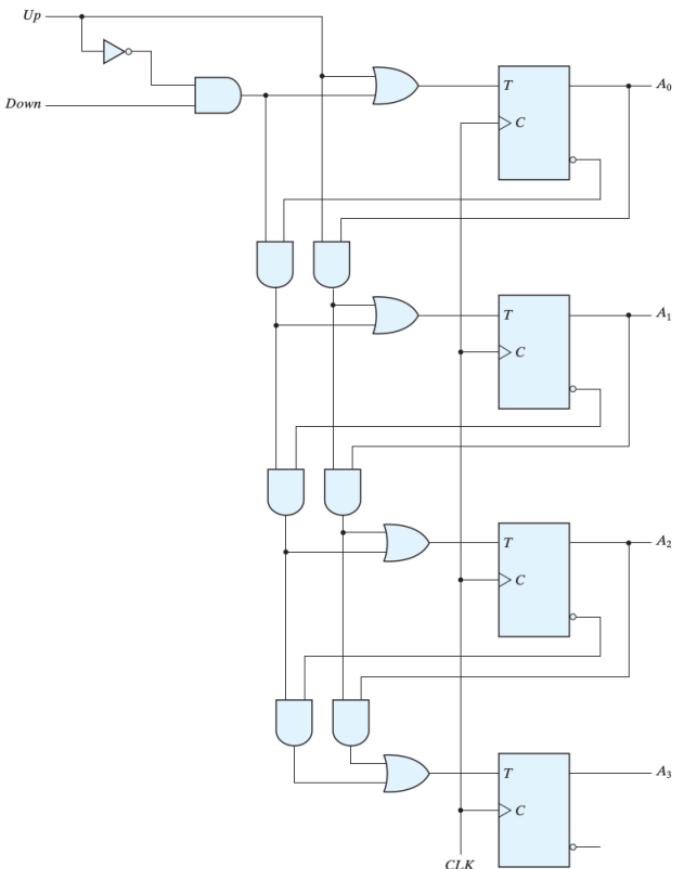 

### 6.2.3 BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$TQ_8$	$TQ_4$	$TQ_2$	$TQ_1$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

- The output  $y = 1$  during ALL the count 9
- $y$  can enable the next stage, if any.
- The unused states are taken as X.
- HW: do unused-state analysis.


$$T_{Q_1} = 1$$

$$T_{Q_2} = Q'_8 Q_1$$


$$T_{Q_4} = Q_2 Q_1$$

$$T_{Q_8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$

$$y = Q_8 Q_1.$$

 
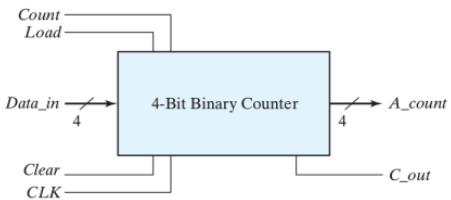
## 6.2.4 Binary Counter with Parallel Load





Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

Other func are possible, e.g., sync clear.


L	C	Function	$J_i$	$K_i$
0	0	no change	0	0
0	1	Up	EqU	EqU
1	X	Load	$I_i$	$I'_i$

$$J_i = L'C \cdot EqU + L \cdot I_i$$

$$K_i = L'C \cdot EqU + L \cdot I'_i$$

  
 
## Example 42 (Design a BCD counter using the Binary Counter with Parallel Load) .





0	0	0	0
0	0	0	0
X	X	X	X
0	1	X	X

$$L = A_3 A_0$$




1	1	1	1
1	1	1	1
X	X	X	X
1	1	X	0

$$C = A'_3 + A'_1 = (A_3 A_1)'$$

  

  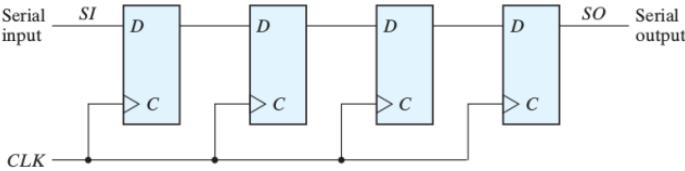
## 6.3 Shift Registers

- Operations in computers are parallel (faster).
- We need sometimes serial processing/communications (slower):
  - phone lines (serial communications)
  - computer processing (less hardware)
- The output will delay by the number of registers.
- Also, we can convert serial input to parallel.
- Stopping transfer is done by controlling clock (as we will see).
- Controlling should NOT be by controlling clock:
  - Not changing clock path
  - delays clocks in fast circuits (GHz and above)
  - Circuit/design-dependent.
- Alternatively, using  $2 \times 1$  MUX with L for each D FF (Sec. 6.1):  
$$D_i = L'A_i + LA_{i-1}, D_0 = L'A_o + LI$$
- Block diagram: serial input (I), serial output (O), clock (C), and transfer control (L).


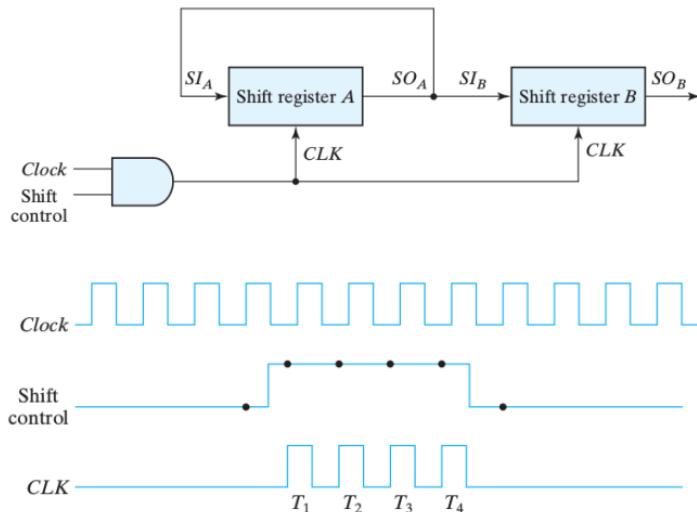
### 6.3.1 Serial Transfer (compare to parallel registers 6.1)

- Notice: the control signal width = the register size (4 here).
- The control signal should be synchronized with clock
- Designing the control circuit of registers is a major part of computer organization (the second major part is designing the circuits themselves, e.g., ALU)
- Example:** Initial value of A and B:




Timing Pulse	Shift Register A				Shift Register B				
Initial value	1	0	1	1		0	0	1	0
After $T_1$	1	1	0	1		1	0	0	1
After $T_2$	1	1	1	0		1	1	0	0
After $T_3$	0	1	1	1		0	1	1	0
After $T_4$	1	0	1	1		1	0	1	1

### 6.3.2 Serial Addition
 
#### Design 1 (modular):

- Recall the parallel adder of Sec. 4.5.4 to see the trade-off between hardware complexity and speed.
- The serial adder adds one-bit at a time.
- $A = A + SI$  (cumulatively).
- Initially:  $A = 0, B = SI$ .
- After  $n$  cycles:  $A = A + 0$  and  $B = \text{new } SI$ .
- Controlling the FF should be by “Load” as explained.
- The next carry-in ( $z$ ) is the current carry-out ( $C$ )  $\Rightarrow$  a delay caused by a D FF.
- Now:** Had not we realized this trick, could we design from scratch? Yes we can but longer and harder. Lets see (with keeping in mind from the FA (4.5.2) that):

$$C = Qx + Qy + xy$$
$$S = x \oplus y \oplus Q.$$



## Design 2 (longer):

- The summation  $x + y$  depends on the carry (0 or 1) so it should be represented by a state  $Q$  of a single FF; draw the truth table:

- Using D FF:

$$D = Q(t+1) = Qx + Qy + xy$$

$$S = x \oplus y \oplus Q.$$

Present State		Inputs		Next State		Output		Flip-Flop Inputs	
<b>Q</b>		<b>x</b>	<b>y</b>	<b>Q</b>		<b>S</b>		<b>J<sub>Q</sub></b>	<b>K<sub>Q</sub></b>
0		0	0	0		0		0	X
0		0	1	0		1		0	X
0		1	0	0		1		0	X
0		1	1	1		0		1	X
1		0	0	0		1		X	1
1		0	1	1		0		X	0
1		1	0	1		0		X	0
1		1	1	1		1		X	0


exactly the same as the outputs C and S of the FA in design 1.  
 (A redesign for the FA of Sec. 4.5.2!!)

- Using JK FF:

$$J = xy,$$

$$K = (x + y)',$$

$$S = x \oplus y \oplus Q.$$

 



### 6.3.3 Universal Shift Register

- For shift right, the MSB (w.r.t.  $A_3A_2A_1A_0$ ) or the LSB (w.r.t. SI) should be the input to the MUX.

- Vise versa for shift left.

#### Mode Control

<b>s<sub>1</sub></b>	<b>s<sub>0</sub></b>	<b>Register Operation</b>
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

  

## 6.4 Ripple Counters

### 6.4.1 Binary Ripple Counters (all counts exist) recall synchronous 6.2.1

**Hint:** all toggles at -ve edge (even  $T_o$ ) because in counting,  $A_i$  toggles when  $A_{i-1}$  goes from 1 to 0



$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

**Using T FF:**  $Clk_i = A'_{i-1}$ ,  $Clk_0 = Clk'$ ,  $T_i = 1$ .

**Using D FF:**  $Clk_i = A'_{i-1}$ ,  $Clk_0 = Clk'$ ,  $D_i = A'_i$

**Advantages:** clock divider, counter, simpler (less hardware, and hence power consumption).

  **Disadvantages:** clock ripples (propagates) and hence delays; so number of stages ( $n$ ) is restricted. Design is very tricky for non binary counters (see BCD next:)



## **Delay comparison between synchronous and ripple counters:**

Suppose that the FF delay is  $\Delta_1$ , the AND delay is  $\Delta_2$ , the clock period is  $T$ , and # of FFs is  $n_r, n_s$ , respectively.

### **Ripple:**

$A_0$  appears after  $\Delta_1$

$A_1$  appears after  $\Delta_1 + \Delta_1 = 2\Delta_1$ , and so on...

Then,  $A_{n_r-1}$  appears after  $n_r\Delta_1$ .

The last bit should appear before  $T$  (the next edge)  $\Rightarrow n_r\Delta_1 < T$ .

### **Synchronous: (Sec. 6.2.1)**

All  $A_i$  appears after  $\Delta_1$  (since clock is common).

However, the input to  $n^{\text{th}}$  FF suffers from  $n_s - 1$  delays of AND gates.  $\Rightarrow (n_s - 1)\Delta_2 < T$

Almost,  $\Delta_1 > 2\Delta_2$  (because the FF master-slave latch has at least 2-level gates (Sec. 5.3.2));  
 $\Rightarrow n_s > 2n_r \Rightarrow$  # of counts will be more than squared.

## 6.4.2 BCD Ripple Counters

Recall the counting mechanism of BCD synchronous counters 6.2.3:

Present State			
$Q_8$	$Q_4$	$Q_2$	$Q_1$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

X	1	1	X
X	1	1	X
X	X	X	X
X	0	X	X

$$J_2 = Q'_8$$

X	0	0	X
X	0	1	X
X	X	X	X
X	X	X	X

$$J_8 = Q_4 Q_2$$

All FFs should either flip or reset  $\Rightarrow K_i = 1$  and  $J_i$  either 0 or 1

If  $Q_i$  feeds the clock of a FF  $\Rightarrow$  at +ve edges no transition  $\Rightarrow$  X.


**FF1:** flips when  $Ck : 1 \rightarrow 0 \Rightarrow C_1 = Ck'$  AND no exception  $\Rightarrow J = 1$

**FF2:** flips when  $Q_1 : 1 \rightarrow 0 \Rightarrow C_2 = Q'_1$ , AND at 9  $Q_2 : 0 \rightarrow 0 \Rightarrow J_2 = 0$

**FF4:** flips when  $Q_2 : 1 \rightarrow 0 \Rightarrow C_4 = Q'_2$ , AND no exception  $\Rightarrow J_4 = 1$

**FF8:** flips when  $Q_1 : 1 \rightarrow 0 \Rightarrow C_8 = Q'_1$ , AND:

 at 7 ( $Q_8 : 0 \rightarrow 1 \Rightarrow J_8 = 1$ ) OR at 9 ( $Q_8 : 1 \rightarrow 0 \Rightarrow J_8 = X$ )



## 6.5 Other Counters

### 6.5.1 Ring Counters

In control units, we need to keep track of the order of  $2^n$  clock pulse (in which cycle we are now in?) Only one wire of the  $2^n$  will be one at a clock cycle.

**Design 1** (ring counter):


$2^n$ -bit shift register with initially “1000…”

=>  $2^n$  FFs

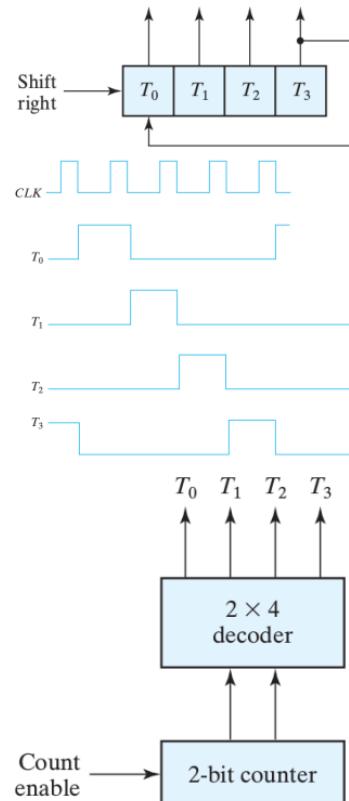
**Design 2 :**

one  $n$ -bit binary counter + one  $n \times 2^n$ -decoder

=> ( $n$  FFs +  $2^n$   $n$ -input AND gates).



## 6.5.2 Johnson Counter

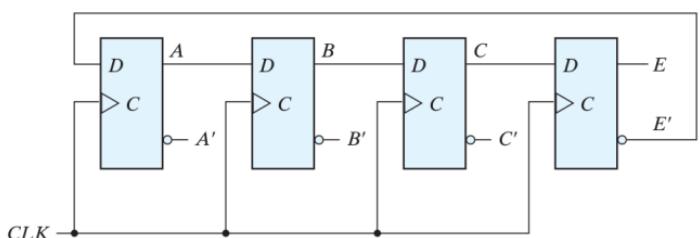

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

**Design 3** : (modified ring counter):

$2^{n-1}$ -bit shift register with initially “00… +  $2^n$  2-input AND gates  
 $\Rightarrow 2^{n-1}$  FFs +  $2^n$  2-input AND gates.

**Advantages** : It is half the number of FFs than the ring counters with additional AND gates. The AND gates are 2-input (to be compared with the  $n$ -input of **Design 2**)

**Disadvantages** : will not get out of any visited unused state!

## **6.6 HDL for Registers and Counters**

# **Homework**

## **Chapter 7**

# **Memory and Programmable Logic**

## 7.1 Introduction

**Motivation** : memory for storing information to be processed by processor

- All circuits designed so far will be part of the processor ALU.
- The second part of the processor is the CU.
- Processor needs to access information to be processed.

**Memory** : collection of cells for storing information (bits) to be fetched from/to processor

- Random-Access Memory (RAM):
  - Storing data (writing)
  - Retrieving data (reading)
  - volatile
- Read-Only Memory (ROM) is a PLD device.


**Programmable Logic Device (PLD)** : programming is a hardware procedure specifying bits inserted into the device for future use. PLD may have 100s–1000,000s of gates.

- Read-Only Memory (ROM)
- Programmable Logic Array (PLA)
- Programmable Array Logic (PAL)
- Field-Programmable Gate Array (FPGA)
 
## 7.2 Random-Access Memory (RAM): block-design

- “Random-Access”: access time is constant
- “Byte”: 8 bits
- “Word”: multiple of bytes
- “Address”: points at word,  $(0) - (2^k - 1)$ .
- “capacity” or “size”: total number of bytes in memory.
- Ex. for 10-bit address and 2-byte word length:

$$\begin{aligned} \text{Size} &= 2^{10} \text{ Words} \\ &= 1024 \text{ Words} \\ &= 1 \text{ K Words} \\ &= 1 \text{ K} \times 2 \text{ Bytes} \\ &= 2 \text{ KB} \end{aligned}$$




Memory address	Binary	Decimal	Memory content
	0000000000	0	1011010101011101
	0000000001	1	1010101110001001
	0000000010	2	0000110101000110
	⋮	⋮	⋮
	1111111101	1021	1001110100010100
	1111111110	1022	0000110100011110
	1111111111	1023	1101111000100101

- $1 \text{ G} = 1024 \text{ M} = 2^{10} \text{ M}$
- $1 \text{ M} = 1024 \text{ K} = 2^{10} \text{ K}$
- $1 \text{ K} = 1024 = 2^{10}$
- $1 \text{ G} = 2^{30}$

## 7.3 Memory Decoding
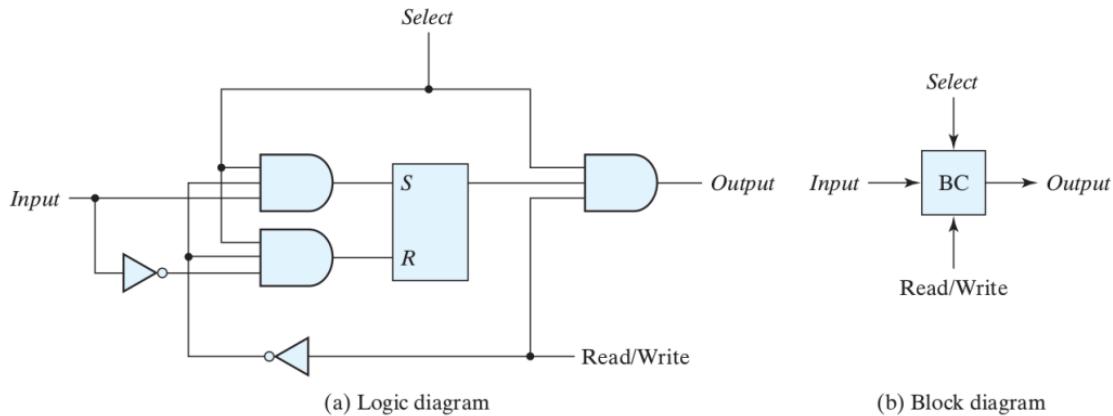
### 7.3.1 Internal Construction of 1-bit RAM




- RAM is fabricated directly not implemented as connected components (this is just a logic diagram)
- Registers vs. RAM (inside processor, sync. with clock, faster, not expandable, etc.)

sel	read	function	output	memory content ( <i>Q</i> )	S	R	
0	X	no. change	no. output	0	no change	0	0
1	0	write	0		changes	I	I'
1	1	read	Q	no change	0	0	$S = \text{sel} \cdot \text{read}' \cdot I$ $R = \text{sel} \cdot \text{read}' \cdot I'$ $\text{output} = \text{sel} \cdot \text{read} \cdot Q$
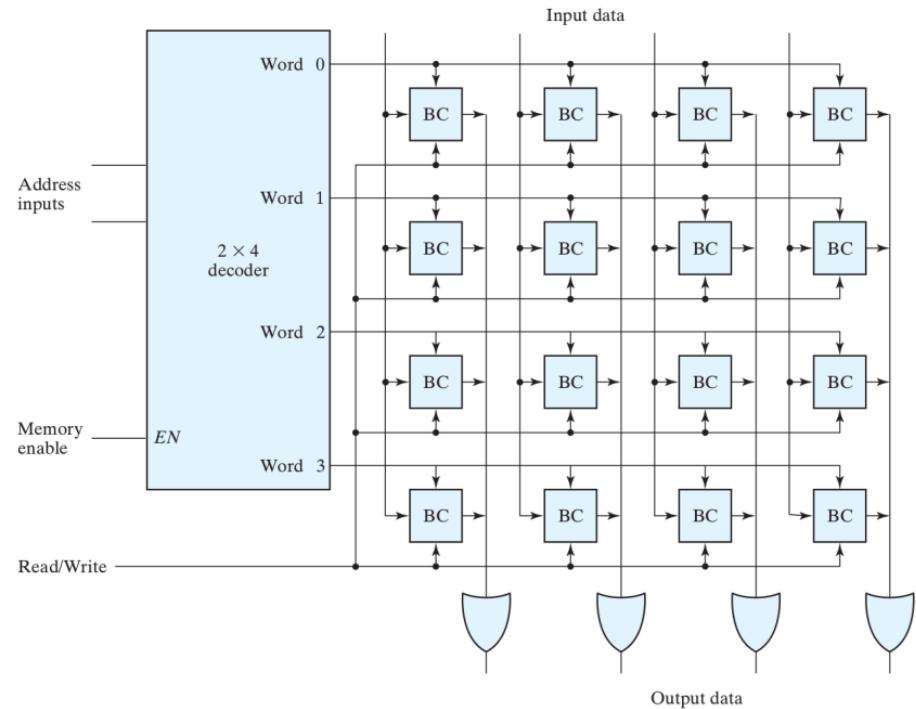
## $2^k$ -words- $n$ -bit RAM:

( $4 \times 4$  in this example)

- The OR gates are represented as array logic.
- Decoder Enable accounts for Enable to the whole memory unit.
- Lets save the hardware of the decoder:




(a) Conventional symbol



(b) Array logic symbol

 
### 7.3.2 Coincident Decoding

- Redesign each BC has 2 selects from 2 decoders (for row/column); and hence each word has two selects.
- So, memory cells are arranged in a matrix (a dot is a word).
- The address now is:  $k/2$  MSBs ( $X$ ) and  $k/2$  LSBs ( $Y$ ).
- $k \times 2^k$ -decoder (prev. design):  $2^k k$ -input AND gates.
- $2(k/2) \times 2^{(k/2)}$ -decoder (coinc. dec.):  $2 * 2^{(k/2)} (k/2)$  - input AND gates.
- $2^k > 2^{1+(k/2)}$  if  $k > 2$ .
- For this decreased HW, can we decrease the # of pins? Lets see:



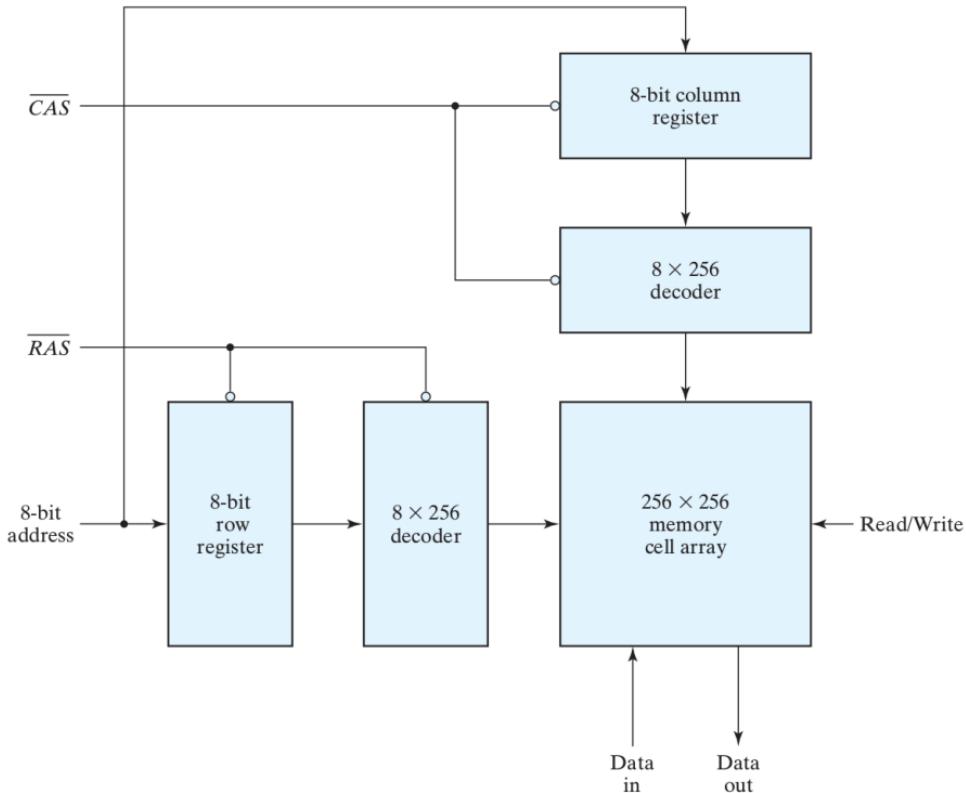
### 7.3.3 Address Multiplexing

- The Row/Column Address Strobe (RAS/CAS) selects the MSB/LSB part of the address line (only  $k/2$ ). A **very smart** trick to reduce the number of pins in the IC is to use only  $k/2$  but in two cycles using 2 registers to save  $X$  and  $Y$ .
- This is always needed in DRAM, which is designed with only one MOS transistor and a capacitor that stores information (but discharges with time; so it needs refreshing); while SRAM BC almost needs 6 transistors;
- DRAM saves: space, cost, power.




## **7.4 Error Detection and Correction**
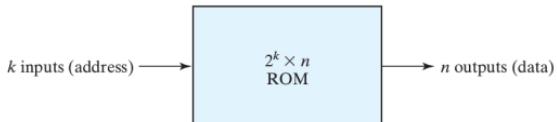
## 7.5 Read-Only Memory (ROM): non-volatile



- Motivation: flash memory and motherboard BIOS.
- ROM: comes programmed from manufacturer (clients provide their truth table)
- PROM: Programmable ROM, is programmed using special burners.
- EPROM: Erasable PROM (erased by ultra-violet application)
- EEPROM: Electrically Erasable PROM, e.g., motherboard bios and flash memory.
- In this example,  $A_i$  is the output of ORing all decoder outputs. The *crosspoints* have fuses all are normally connected to give One (intact and shown as stars \*). When blown up (by high voltage) the *crosspoint* is disconnected to give Zero.

Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	0	0	1	0	1
⋮					⋮							
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 


**Example 43 (7.1) : ROM can be seen as:**

**Storage device** : if we look at the table row-wise. The  $k$ -bit input will select the appropriate row.




**Combinational functions** : if we look at the table column-wise. The  $k$ -bit input has  $n$  corresponding functions  $A_1-A_n$ . For a particular input, each function provides a value.

Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

 



$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

## ROM is one of three types of PLDs:

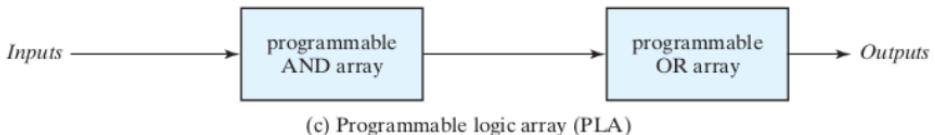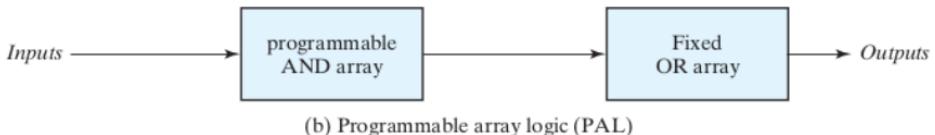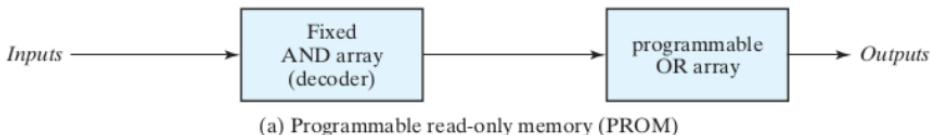


Same concept as ROM; we will just allude to that:
 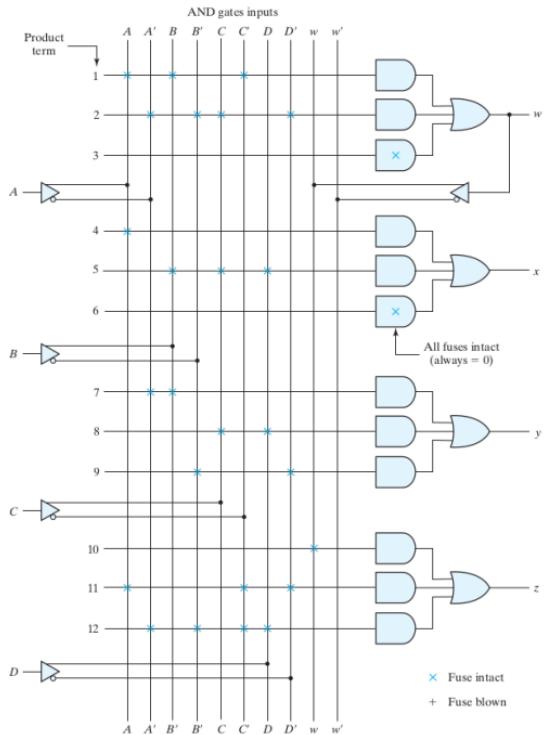
## 7.6 Programmable Array Logic (PAL) 7.7 Programmable Logic Array (PLA)


 
## 7.8 Sequential Programmable Devices: (more advanced topics)

- To add the sequential circuitry to the IC for extending PLD.
- This is a topic that is very advanced for a first course in Digital Design.
- The most important and recent technology is Field-Programmable Gate Array (FPGA).
- It is: VLSI circuit that can be programmed at the user's location.
- An FPGA contains: thousands or more programmable logic blocks.
- A logic block contains: multiplexers, gates, FFs.
- Programming requires extensive HDL coding to describe the required hardware.
- The most famous FPGA is by Xilinx nc. (/zy-lingks)
- Breadboards, Printed Circuit Boards (PCB), FPGA, Fabrication. (Sec. 2.9)



**Xilinx, Spartan 3E:** Summer training, 2008, for top 10 students in digital design. The power and USB-PC connector are shown.

## **Chapter 8**

# **Design at the Register Transfer Level: (a gate to "Computer Organization")**

## 8.1 Introduction

- Remember block design of combinational circuits, e.g., 4.7.2.
- We need the same for sequential circuits; otherwise, we will do state table for hundreds of states.
- When it comes to very large scale integration, it is impossible but block-design.
- Same concept in programming; no one writes high level functions in Assembly.
- We will provide essential tools here in this chapter and leave the rest to the whole course of “Computer Organization”.

## 8.2 Register Transfer Language (RTL)

**Simple examples:** draw datapath vs. control

1. very simple transfer

$$R2 \leftarrow R1$$

2. controlling the transfer (see ring counter 6.5.1 for T3)

$$\text{If } (T3 = 1) \text{ then } R2 \leftarrow R1$$

3. more transfer at same condition

$$\text{If } (T3 = 1) \text{ then } R2 \leftarrow R1, R1 \leftarrow R2$$


4. other transfer and control

$$\text{If } (T2 = 1) \text{ then } R1 \leftarrow R1 + R2$$

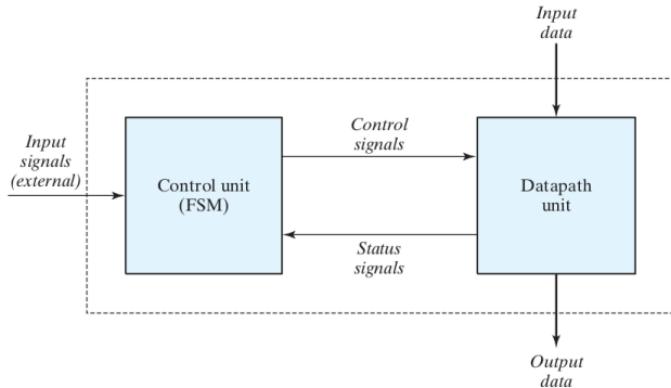5. Here, we need additional MUX and feedback from datapath to control.

$$\text{If } (T2 = 1) \text{ then If } (R1 > 0) \text{ then } R1 \leftarrow R1 + R2$$

$$\text{If } (T3 = 1) \text{ then } R2 \leftarrow R1, R1 \leftarrow R2$$



## **8.3 Register Transfer Language (RTL) in HDL**

# **Homework**

## 8.4 Algorithmic State Machines (ASMs)

**Rectangle box** is a state with name and number. Transitions happens next edge with a “Moore” control, e.g., `incr_A`.

**Diamond box** is a “Mealy” condition.

**Round rectangle** : is a conditional Mealy output that occurs once the condition happens. **However:** the register actions take place next edge of course.

**ASM Block** is therefore a rectangle box, along with all diamonds, and rounded boxes stemming from it. All takes place either during the cycle (Mealy conditions and outputs) or at the next edge (register transfer).




**Asynchronous Start** `Reset_b`.

**ASM vs. Flow Chart** ASM is different in the timing of actions.  $A \leftarrow A + 1$ ,  $R \leftarrow 0$ , and transition to next state **ALL** happens at the end of  $S_0$  at the edge of next clock; while in flow-chart it is executed right away. E.g.,  $R \leftarrow 0$  is in  $S_0$  block; however, it means that the controller is ready during  $S_0$  to cause this transfer at the exit of  $S_0$  (next edge).

**Figures (b), (c)** : datapath and controls.




We can convert the ASM chart to a state diagram for easy design like this one =>

   **ASMD** (Algorithmic State Machine and Datapath) combines both (a) and (b) for very clear design and implementation as will be seen next example:


  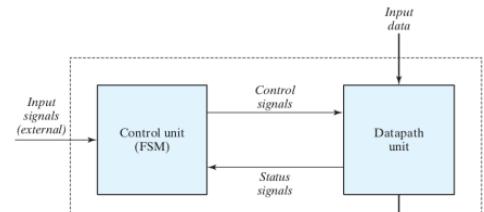
## 8.5 Design Example

- 2 JK FF (E and F), and one 4-bit binary counter ( $A[3 : 0]$ ).
- Start initiates the system: ( $A = 0, F = 0$ ).
- Each clock pulse,  $A$  is incremented.
- If  $A_2 = 0$ , E is cleared and count continues.
- If  $A_2 = 1$ , E is set to 1; then if  $A_3 = 0$ , count continues, but if  $A_3 = 1$ , F is set to 1 on the next clock pulse and system stops counting. Then, if  $Start = 0$ , system remains in the initial state, but if  $Start = 1$  repeat.




# Cont.

- 2 JK FF (E and F), and one 4-bit binary counter ( $A[3:0]$ ).
- Start initiates the system: ( $A = 0, F = 0$ ).
- Each clock pulse,  $A$  is incremented.
- If  $A_2 = 0$ , E is cleared and count continues.
- If  $A_2 = 1$ , E is set to 1; then if  $A_3 = 0$ , count continues, but if  $A_3 = 1$ , F is set to 1 on the next clock pulse and system stops counting. Then, if  $Start = 0$ , system remains in the initial state, but if  $Start = 1$  repeat.


Tracing the ASMD assuming that we come from S\_2:

### Sequence of Operations for Design Example

Counter				Flip-Flops		Conditions	State
$A_3$	$A_2$	$A_1$	$A_0$	$E$	$F$		
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	$S\_I$
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	$S\_2$
1	1	0	1	1	0		
1	1	0	1	1	1		$S\_idle$

 

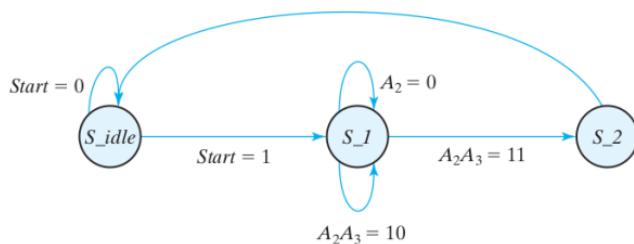
$$\begin{aligned}
D_{G1} &= G'_1 G_0 A_2 A_3 \\
D_{G0} &= \text{Start } G'_1 G'_0 + G'_1 G_0 \\
\text{set\_}_E &= G'_1 G_0 A_2 \\
\text{clr\_}_E &= G'_1 G_0 A'_2 \\
\text{set\_}_F &= G_1 G_0 \\
\text{clr\_}_A\_F &= \text{Start } G'_1 G'_0 \\
\text{incr\_}_A &= G'_1 G_0
\end{aligned}$$



State Table for the Controller of Fig. 8.10

Present-State Symbol	Present State		Inputs		Next State		Outputs					
	$G_1$	$G_0$	$Start$	$A_2$	$A_3$	$G_1$	$G_0$	$\text{set\_}_E$	$\text{clr\_}_E$	$\text{set\_}_F$	$\text{clr\_}_A\_F$	$\text{incr\_}_A$
$S_{idle}$	0	0	0	X	X	0	0	0	0	0	0	0
$S_{idle}$	0	0	1	X	X	0	1	0	0	0	1	0
$S_I$	0	1	X	0	X	0	1	0	1	0	0	1
$S_I$	0	1	X	1	0	0	1	1	0	0	0	1
$S_I$	0	1	X	1	1	1	1	1	0	0	0	1
$S_2$	1	1	X	X	X	0	0	0	0	1	0	0

 

$$D_{G1} = G'_1 G_0 A_2 A_3$$

$$D_{G0} = Start \ G'_1 G'_0 + G'_1 G_0$$



$$set\_E = G'_1 G_0 A_2$$

$$clr\_E = G'_1 G_0 A'_2$$

$$set\_F = G_1 G_0$$

$$clr\_A\_F = Start \ G'_1 G'_0$$

$$incr\_A = G'_1 G_0$$

  



## **Appendix A**

# **Numbering System and Binary Numbers**

## **Appendix B**

# **Boolean Algebra**

## **Appendix C**

# **Digital Integrated Circuits (ICs)**

# Bibliography

- Mano, M. M., Ciletti, M. D., 2007. Digital design, 4th Edition. Prentice-Hall, Upper Saddle River, NJ.
- Patterson, D. A., Hennessy, J. L., 2007. Computer Organization And Design : The Hardware/Software Interface, 3rd Edition. MORGAN KAUFMANN, Boston.
- Rosen, K. H., 2007. Discrete mathematics and its applications, 6th Edition. McGraw-Hill Higher Education, Boston.
- Sipser, M., 2006. Introduction to the theory of computation, 2nd Edition. Thomson Course Technology, Boston.